

1Ph_FW_Inverter_R-L_Load -- Overview



Dr. Ashish Shrivastava (Professor & HoD)

Vikas Singh Bhadoria (Asst. Professor)

Electrical Engineering Department
JRE Group of Institution, Gr.Noida (UP)



1-PHASE FULL-WAVE INVERTER WITH R-L LOAD

Objective:

After performing this lab exercise, learner will be able to:


- Understand the working of DC-AC inverter
- Learn the role of Power Electronics in utility related applications.
- Understand and design single-phase Full Wave Inverter with R-L Load.
- Analyze and interpret results
- Work with digital oscilloscope to debug circuit and analyze signals

Equipment:

To carry out this experiment, you will need:

- Single phase inverter kit
- SCR firing circuit kit, 1-phase, 230V, 5A
- Patch chords
- Load
- Digital Oscilloscope


Circuit Diagram:

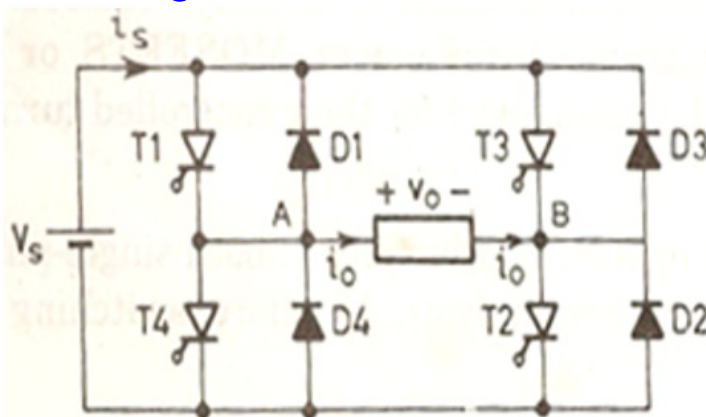

Theory:

- Single phase full bridge inverter consists of four SCRs and four diodes. For Full bridge inverter when T1, T2 conduct, load voltage is V_s and T3, T4 conduct load voltage is $-V_s$.

- Frequency of output voltage can be controlled by varying the periodic time T .
- During inverter operation it should be ensured that two thyristors in the same branch should not conduct simultaneously as this would lead to a direct short circuit of the source.
- For inductive load, load voltage and load current will not be in phase with each other. In this case diodes D_1 , D_2 , D_3 and D_4 connected in antiparallel will thyristors will allow the current to flow when main thyristors are turned off. As the energy is fed back to the dc source when these diodes conduct, these are called feedback diodes.
- Before $t = 0$, thyristors T_3 and T_4 are conducting and load current i_0 is flowing from B to A, i.e. in reverse direction. This current is $-i_0$ at $t = 0$.
- After T_3 and T_4 are turned off at $t = 0$, current i_0 cannot change its direction immediately because of the nature of load.
- As a result diodes D_1 and D_2 starts conducting after $t = 0$ and allow i_0 to flow against the supply voltage V_s . As soon as D_1 and D_2 begin to conduct, load is subjected to V_s .
- Though T_1 and T_2 are gated at $t = 0$, these SCRs will not turn on as these are reverse biased by voltage drop across diodes D_1 and D_2 .
- When Load current through D_1 and D_2 falls to zero, T_1 and T_2 becomes forward biased by source voltage V_s .
- Now T_1 and T_2 get turned on as these are gated for the period of $T/2$ seconds. Now load current i_0 flows in the positive direction from A to B. At $t = T/2$; T_1 and T_2 are turned off by forced commutation and as load current cannot reverse immediately, diodes D_3 and D_4 come into conduction to allow the flow of current i_0 after $T/2$.
- Thyristor T_3 and T_4 though gated will not turn on as these are reverse biased by the voltage drop in diodes D_3 and D_4 . When current in diodes D_3 and D_4 drops to zero; T_3 and T_4 are turned on as these are already gated.
- The ideal waveform of the experimental setup is shown in Figure below:

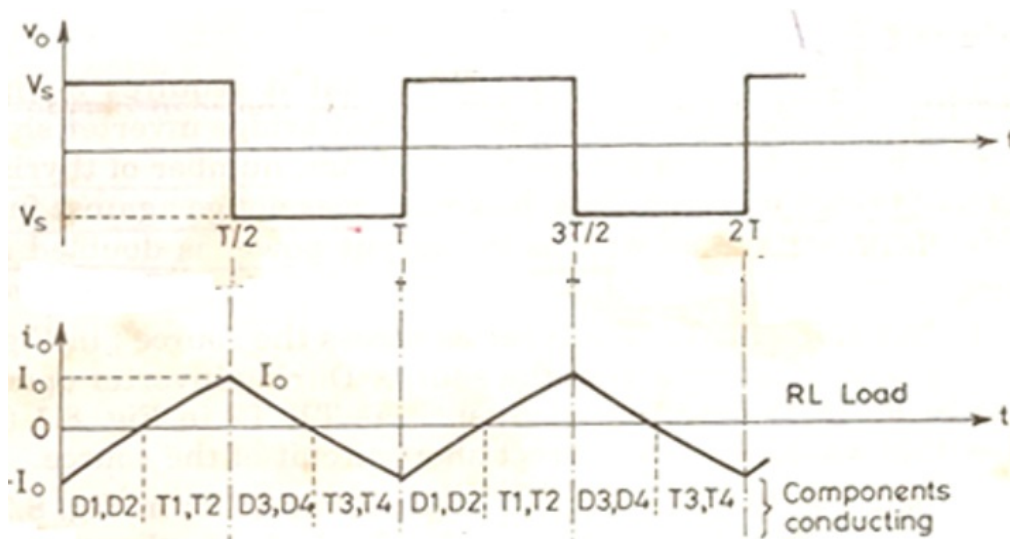

1Ph_FW_Inverter_R-L_Load -- Procedures

Step 1


Precautions:

- A main switch should be included in whole circuit, so that in case of any emergency main supply can be disconnected from the circuit.
- Check all the connection before switching ON the power supply.
- Apply low voltages or low power to check the proper functionality of circuits.
- Load should be remained connected to the experimental setup for discharging the energy stored in the inductor or capacitor present in the circuit, if any.
- Don't touch live wires.

Step 2

Circuit Setup:

Build the circuit as shown below:

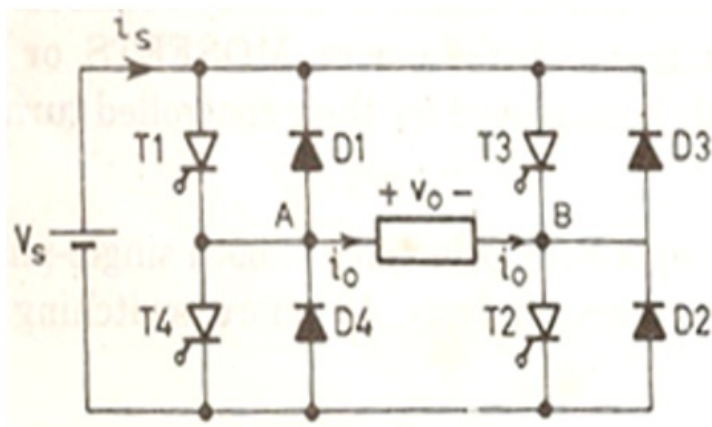

Step 3

Probe across load resistance (V_0)

Step 4

Keep the multiplication factor of the CRO's probe at the maximum position (10X or 100X - whichever is available)

Step 5

Switch on the experimental kit and firing circuit kit.

Step 6

- Set the duty cycle to 50%
- Capture output waveform on oscilloscope

Step 7

- Measure the RMS value of the output
- Take screenshot of output waveform.

Step 8

Switch off the power supply and disconnect from the power source.