

# 1Ph\_FW\_Inverter\_RLC\_Load -- Overview



Dr. Ashish Shrivastava (Professor & HoD)

Vikas Singh Bhadoria (Asst. Professor)

Electrical Engineering Department  
JRE Group of Institution, Gr.Noida (UP)



## 1-PHASE FULL-WAVE INVERTER WITH R-L-C LOAD

### Objective:

After performing this lab exercise, learner will be able to:


- Understand the working of DC-AC inverter
- Learn the role of Power Electronics in utility related applications.
- Understand and design single-phase Full Wave Inverter.
- Understand the concept of underdamping and over-damping
- Analyze and interpret results
- Work with digital oscilloscope to debug circuit and analyze signals

### Equipment:

To carry out this experiment, you will need:

- Single phase inverter kit
- SCR firing circuit kit, 1-phase, 230V, 5A
- Patch chords
- Load
- Digital Oscilloscope

### Circuit Diagram:

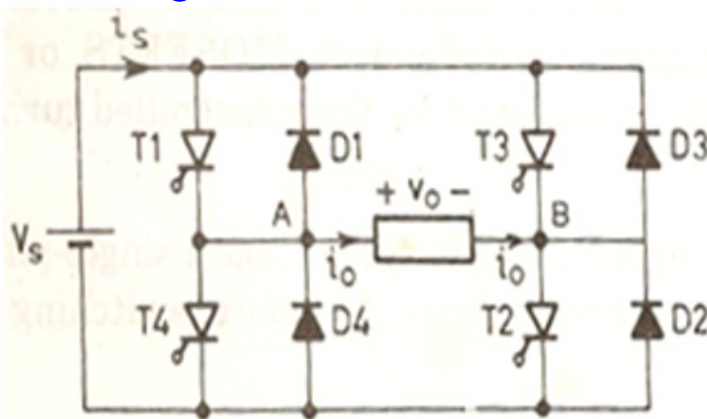


### Theory:

- Single phase full bridge inverter consists of four SCRs and four diodes. For Full bridge inverter when T1, T2 conduct, load voltage is  $V_s$  and T3, T4 conduct load voltage is  $-V_s$ .

- Frequency of output voltage can be controlled by varying the periodic time  $T$ .
- During inverter operation it should be ensured that two thyristors in the same branch should not conduct simultaneously as this would lead to a direct short circuit of the source.
- For inductive load, load voltage and load current will not be in phase with each other. In this case diodes  $D_1$ ,  $D_2$ ,  $D_3$  and  $D_4$  connected in antiparallel will thyristors will allow the current to flow when main thyristors are turned off. As the energy is fed back to the dc source when these diodes conduct, these are called feedback diodes.
- Operation of series R-L-C load can be explained for R-L-C under damped and over damped load.
- **R-L-C Over Damped Load:**
  - Before  $t = 0$ , thyristors  $T_3$  and  $T_4$  are conducting and load current  $i_o$  is flowing from B to A, i.e. in reverse direction. This current is  $-i_o$  at  $t = 0$ .
  - After  $T_3$  and  $T_4$  are turned off at  $t = 0$ , current  $i_o$  cannot change its direction immediately because of the nature of load. As a result diodes  $D_1$  and  $D_2$  starts conducting after  $t = 0$  and allow  $i_o$  to flow against the supply voltage  $V_s$ . As soon as  $D_1$  and  $D_2$  begin to conduct, the load is subjected to  $V_s$ .
  - Though  $T_1$  and  $T_2$  are gated at  $t = 0$ , these SCRs will not turn on as these are reverse biased by the voltage drop across the diodes  $D_1$  and  $D_2$ . When Load current through  $D_1$  and  $D_2$  falls to zero,  $T_1$  and  $T_2$  becomes forward biased by source voltage  $V_s$ .
  - Now  $T_1$  and  $T_2$  get turned on as these are gated for the period of  $T/2$  seconds. Now load current  $i_o$  flows in the positive direction from A to B. At  $t = T/2$ ;  $T_1$  and  $T_2$  are turned off by forced commutation and as load current cannot reverse immediately, diodes  $D_3$  and  $D_4$  come into conduction to allow the flow of current  $i_o$  after  $T/2$ .
  - Thyristor  $T_3$  and  $T_4$  though gated will not turn on as these are reverse biased by the voltage drop in diodes  $D_3$  and  $D_4$ . When the current in diodes  $D_3$  and  $D_4$  drops to zero;  $T_3$  and  $T_4$  are turned on as these are already gated
- **R-L-C Over Damped Load:**
  - For R-L-C under damped load after  $t = 0$ , thyristor  $T_1$  and  $T_2$  are carrying load current  $i_o$ . As  $i_o$  through  $T_1$  and  $T_2$  reduces to zero at  $t_1$ , these SCRs are turned off before  $T_3$  and  $T_4$  are gated.
  - As  $T_1$  and  $T_2$  stops conducting, current through the load reverses and now is carried by diodes  $D_1$  and  $D_2$  as  $T_3$  and  $T_4$  are not yet gated.
  - The diodes  $D_1$  and  $D_2$  are connected in antiparallel to  $T_1$  and  $T_2$ ; the voltage drop in these diodes appears as a

reverse bias across T1 and T2.

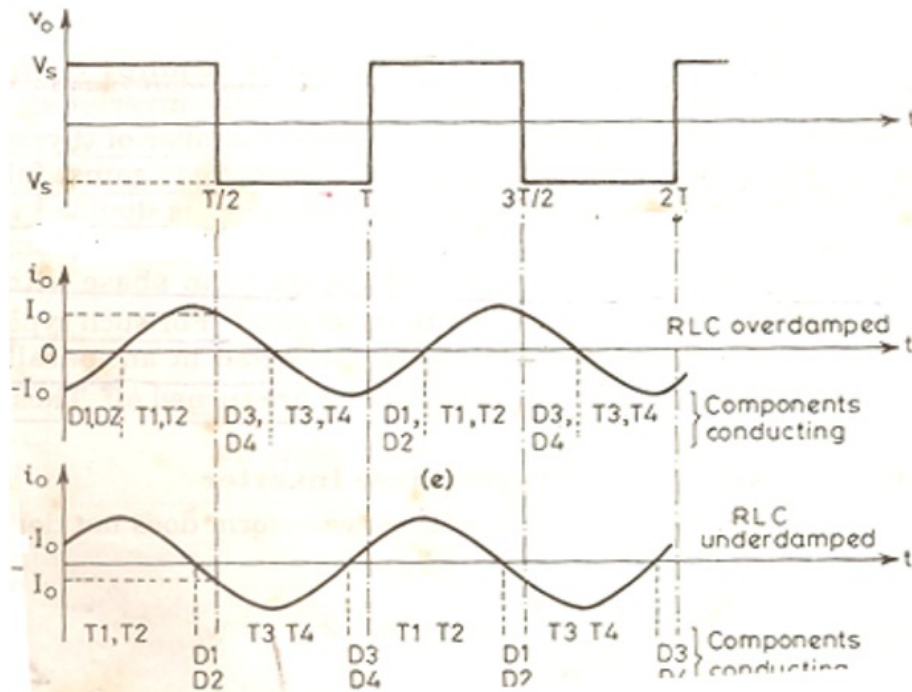- If the duration of reverse bias is more than the SCR turn off time; T1 and T2 will get commutated naturally and therefore no commutation circuitry is needed.
- This method of commutation is known as load commutation.
- The ideal waveform of the experimental setup is shown in Figure below:



## 1Ph\_FW\_Inverter\_RLC\_Load -- Procedures

### Step 1


#### Precautions:

- A main switch should be included in whole circuit, so that in case of any emergency main supply can be disconnected from the circuit.
- Check all the connection before switching ON the power supply.
- Apply low voltages or low power to check the proper functionality of circuits.
- Load should be remained connected to the experimental setup for discharging the energy stored in the inductor or capacitor present in the circuit, if any.
- Don't touch live wires.

### Step 2

#### Circuit Setup:

Build the circuit as shown below:

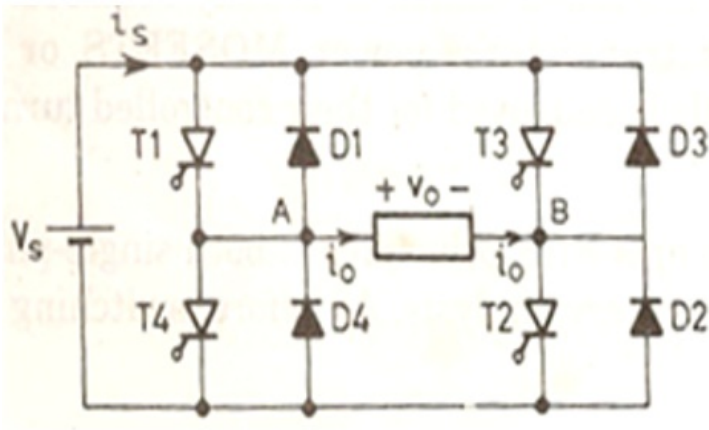

### Step 3

Probe across load resistance ( $V_o$ )

### Step 4

Keep the multiplication factor of the CRO's probe at the maximum position (10X or 100X - whichever is available)

### Step 5

Switch on the experimental kit and firing circuit kit.

### Step 6

- Set the duty cycle to 50%
- Capture output waveform on oscilloscope

### Step 7

- Measure the RMS value of the output
- Take screenshot of output waveform.

### Step 8

Switch off the power supply and disconnect from the power source.