

# 1Ph\_HW\_Inverter -- Overview



**Dr. Ashish Shrivastava** (Professor & HoD)

**Vikas Singh Bhadoria** (Asst. Professor)

Electrical Engineering Department  
JRE Group of Institution, Gr.Noida (UP)



## 1-PHASE HALF WAVE INVERTER WITH R-LOAD

### Objective:

After performing this lab exercise, learner will be able to:


- Understand the working of DC-AC inverter
- Learn the role of Power Electronics in utility related applications.
- Understand and design single-phase Half Wave Inverter.
- Analyze and interpret results
- Work with digital oscilloscope to debug circuit and analyze signals

### Equipment:

To carry out this experiment, you will need:

- Single phase inverter kit
- SCR firing circuit kit, 1-phase, 230V, 5A
- Patch chords
- Load (100 ohm / 2A)
- Digital Oscilloscope

### Circuit Diagram:

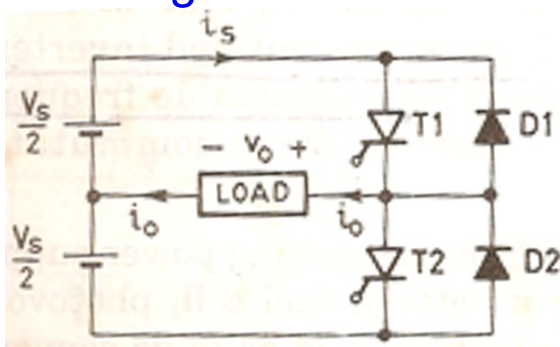


### Theory:

- A device that converts DC power into AC power at desired output voltage and frequency is called an inverter.
- The single phase half bridge consists of two SCRs and two diodes and three wire supply. For  $0 < t \leq T/2$ , thyristor T1 conducts and load is subjected to a voltage  $V_s/2$  due to upper voltage source  $V_s/2$ .
- At  $t = T/2$ , thyristor T1 commuted and T2 is gated on. During the period  $T/2 < t \leq T$ , thyristor T2 conducts and load is subjected to

a voltage ( $-V_s/2$ ) due to lower voltage source  $V_s/2$ .

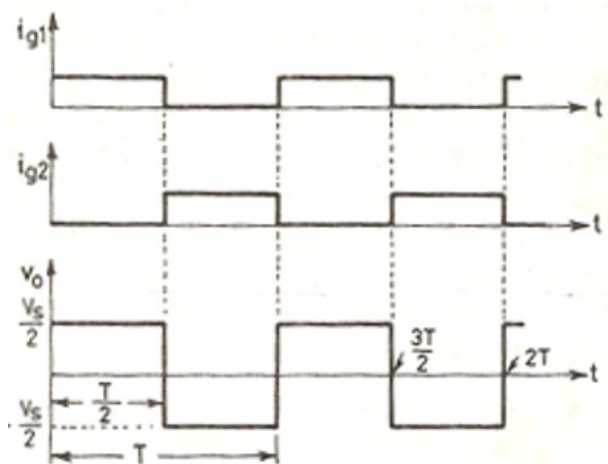- Load voltage is an alternating voltage of amplitude of  $V_s/2$  and of frequency  $1/T$  Hz.
- The frequency of the inverter output voltage can be changed by controlling  $T$ .
- The main drawback of half-bridge inverter is that it requires 3-wire DC supply
- The ideal waveform of the experimental setup is shown in Figure below:



## 1Ph\_HW\_Inverter -- Procedures

### Step 1


#### Precautions:

- A main switch should be included in whole circuit, so that in case of any emergency main supply can be disconnected from the circuit.
- Check all the connection before switching ON the power supply.
- Apply low voltages or low power to check the proper functionality of circuits.
- Load should be remained connected to the experimental setup for discharging the energy stored in the inductor or capacitor present in the circuit, if any.
- Don't touch live wires.

### Step 2

#### Circuit Setup:

Build the circuit as shown below:

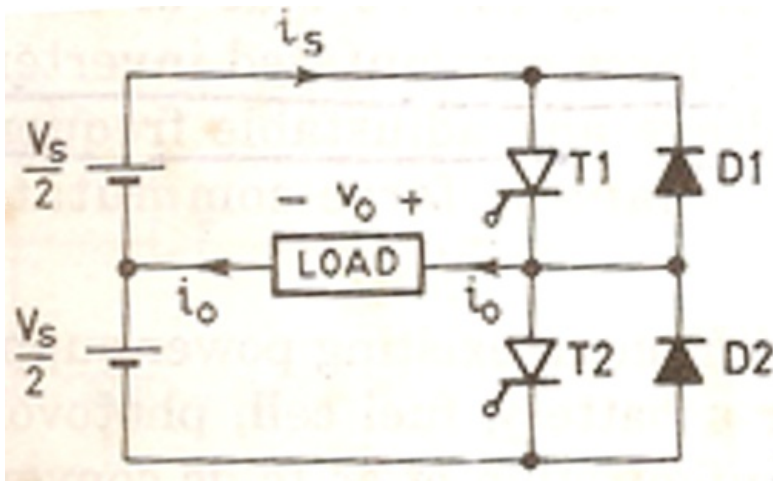

### Step 3

Probe across load resistance ( $V_0$ )

### Step 4

Keep the multiplication factor of the CRO's probe at the maximum position (10X or 100X - whichever is available)

### Step 5

Switch on the experimental kit and firing circuit kit.

### Step 6

- Set the duty cycle to 50%
- Capture output waveforms on oscilloscope

### Step 7

- Measure the RMS value of the output
- Take screenshot of output waveform.

### Step 8

Switch off the power supply and disconnect from the power source.