

ActiveBandPassFilter -- Overview



Dr. B Kanmani

Department Head,
Telecommunication Engineering

BMS College of Engineering (BMSCE),
Bangalore, India



OBJECTIVES:

At the end of performing this experiment, learners would be able to:

- Describe the concept of active Wide Band Pass Filter
- Obtain the Bandwidth and cutoff frequency of the filter designed
- Compare the designed cut-off frequency with the desired cut-off frequency
- Understand the working of $\mu A741$ IC (Op Amp)

EQUIPMENT:

- IC $\mu A741$
- Signal generator
- Resistors
- Capacitor
- +/- 15V DC Power Supply
- Digital Storage Oscilloscope & probes
- Connecting wires & Bread Board

DESIGN:

- Given second order active wide-band-pass filter with a lower cut-off frequency 3KHz, and the upper cut-off-frequency of 30 KHz, having voltage gain of 25.

- Given the lower cut-off frequency f_l Hz, compute the values of the resistor and the capacitor of the HPF, Choose $C = 0.1\mu F$, compute R_l

$$f_{H-BPF} = \frac{1}{2\pi R_l C_l}$$

- Given the upper cut-off frequency f_h Hz, compute the values of the resistor and the capacitor of the LPF, Choose $C = 0.1\mu F$, compute R_h

$$f_{L-BPF} = \frac{1}{2\pi R_h C_h}$$

- Given the gain of the BPF, assume R_1 and compute R_2 using

equation

$$\text{Gain} = \left(1 + \frac{R_2}{R_1}\right)$$

THEORY:

- The μA741 device is a general-purpose operational amplifier featuring offset-voltage null capability
- Band pass filters have a frequency response as shown in figure 1. The difference between the two cut-off frequencies f_L (the lower cut-off) and f_H (the upper cut-off) is known as the bandwidth B_w .

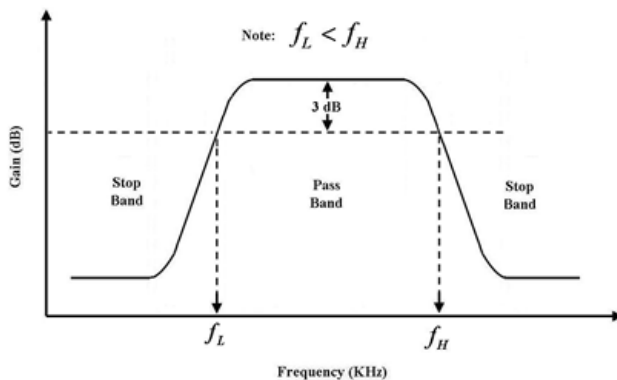


Figure 1: Frequency response of a band-pass filter

- Wide-BPF can be realized by cascading a low-pass and a high-pass filter as shown in figure 2. This method is not economical in terms of use of components, and also when the bandwidth is narrow.

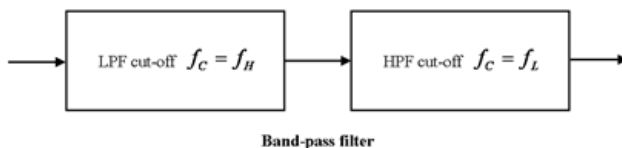


Figure 2: Realization of a band-pass filter

Reference reading:

- 1) Theory and application of Digital Signal Processing, by Lawrence R Rabin and Bernard Gold, Prentice Hall, Easter Economy Edition
- 2) Integrated Electronics, by Millman and Halkias, Tata McGraw-Hill

Acknowledgement


Mr. Shreenivas B for converting laboratory experiment to Tektronix courseware format

ActiveBandPassFilter -- Procedures

Step 1

Circuit setup:

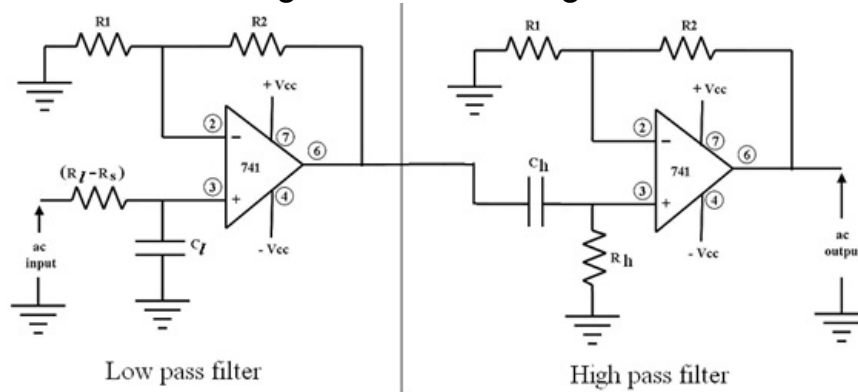Build the following circuit with designed values



Realization of a wide-band-pass filter

Step 2

- Use a signal generator to generate analog input . The analog input will be set to 1 Vpp Sine wave
- Turn on the supply of the circuit and enable signal generator that is feeding signal to the circuit.

Step 3

- Connect the DSO probe – CH1 at analog input (Sine wave), CH2 at output (pin # 6 of $\mu A741$ IC)
- Perform Autoset on DSO and capture the output signal of LPF and verify it

Step 4

- Perform Autoset on DSO and capture the output signal of HPF and verify it

Step 5

- Cascade the two circuit then capture the output signal of BPF

Step 6

- Configure PEAK-to-PEAK measurement on the input and output signal
- Observe and record the signal – input and output.


Step 7

Record the input and output peak-to-peak voltage for various input frequencies, and complete the table below.

Frequency (Hz)	Vin(v)	Vout(v)	Gain (dB) = $20 \log (V_{out} / V_{in})$
100 Hz			
200 Hz			
1MHz			

Step 8

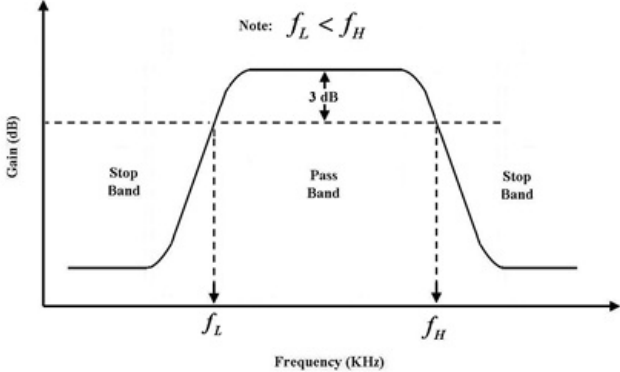Plot the frequency response of the designed filter (Plot of Frequency Vs. Gain on a semi-log sheet), and hence obtain the lower and upper cut-off frequencies



Step 9

Observations:

- i) The designed filter has a lower cut-off frequency(f_l)Hz
- ii) The designed filter has a upper cut-off-frequency (f_h)Hz
- iii) The designed filter has a BandwidthHz

Step 10

Open-ended Question / Can you answer this?

What will be the result if:

- 1) We increase the gain of the BPF ?
- 2) We take capacitor value $1\mu\text{F}$ instead of $0.1\mu\text{F}$?