

ActiveHighPassFilter -- Overview



Dr. B Kanmani
Department Head,
Telecommunication Engineering

BMS College of Engineering (BMSCE),
Bangalore, India



OBJECTIVES:

At the end of performing this experiment, learners would be able to:

- Describe the concept of active High Pass butterworth Filter
- Obtain the roll-off factor and cutoff frequency of the filter designed
- Compare the designed cut-off frequency with the desired cut-off frequency
- Understand the working of $\mu A741$ IC (Op Amp)

EQUIPMENT:

- IC $\mu A741$
- Signal generator
- Resistors
- Capacitor
- +/- 15V DC Power Supply
- Digital Storage Oscilloscope & probes
- Connecting wires & Bread Board

DESIGN:

- Given cut-off frequency f Hz, assume suitable R , and obtain C using equation

$$f_c = \frac{1}{2\pi RC} \text{ Hz}$$

- Assume R_1 and compute R_2 using equation

$$A_F = \left(1 + \frac{R_2}{R_1} \right) = 1.586$$

THEORY:

- Op - Amp is a DC-coupled high-gain electronic voltage amplifier with a differential input and a output.
- The $\mu A741$ device is a general-purpose operational amplifier featuring offset-voltage null capability
- The low pass filter becomes a high pass filter when the Resistor

and Capacitor are interchanged.

Reference reading:

- 1) Theory and application of Digital Signal Processing, by Lawrence R Rabin and Bernard Gold, Prentice Hall, Eastern Economy Edition
- 2) Integrated Electronics, by Millman and Halkias, Tata McGraw-Hill

Acknowledgement


Mr. Shreenivas B for converting laboratory experiment to Tektronix courseware format

Active High Pass Filter -- Procedures

Step 1

Circuit setup:

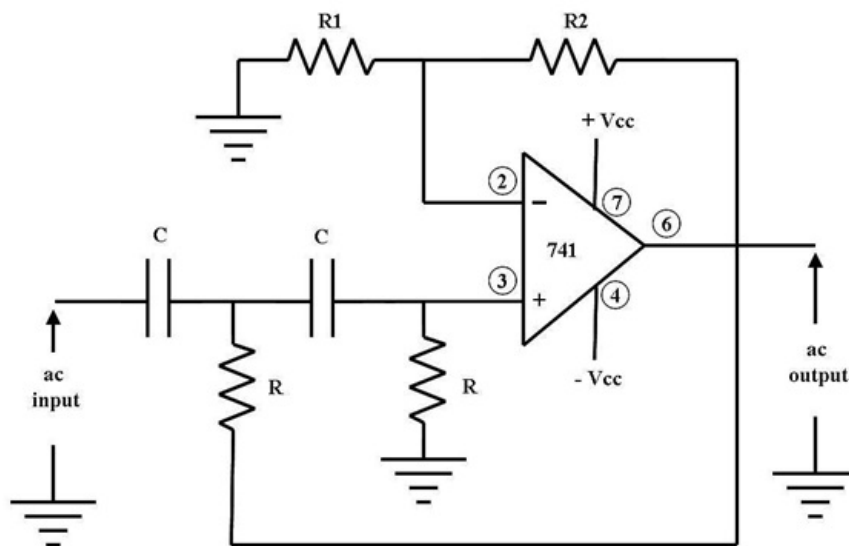Build the following circuit with given designed values



Active second order High pass filter

Step 2

- Use a signal generator to generate analog input. The analog input will be set to 1 Vpp Sine wave
- Turn on the supply of the circuit and enable signal generator that is feeding signal to the circuit.

Step 3

- Connect the DSO probe – CH1 at analog input (Sine wave), CH2 at output (pin # 6 of $\mu A741$ IC)
- Perform Autoset on DSO and capture the output signal.

Step 4

- Configure PEAK-to-PEAK measurement on the input and output signal.
- Observe and record the signal – input and output.


Step 5

Record the input and output peak-to-peak voltage for various input frequencies, and complete the table below

Frequency (Hz)	V input (v)	V output (v)	Gain (dB) = $20 \log (V_{out} / V_{in})$
100Hz			
200Hz			
.....			
1KHz			
2KHz			
.....			
10KHz			
20KHz			
.....			
100KHz			
200KHz			
1MHz			


Step 6

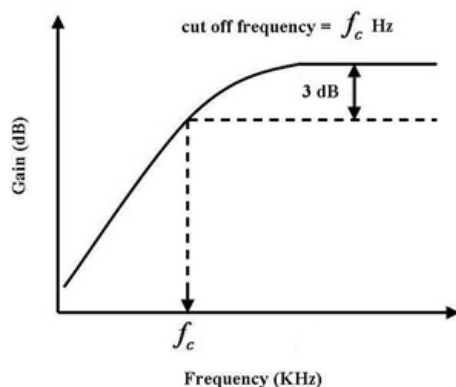Plot the frequency response of the designed filter (Plot of Frequency Vs. Gain on a semi-log sheet), and hence obtain the cut-off frequency



Step 7

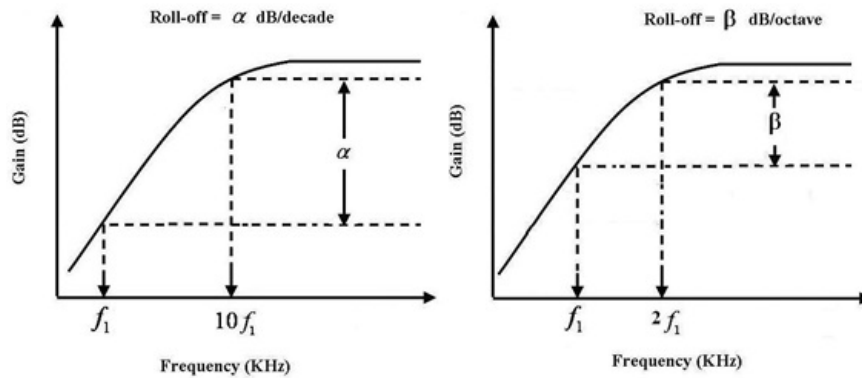Compute the Roll-off factor of the designed filter (The ideal value of roll-off factor is + 40dB/decade or +12dB/octave)



Step 8

Observations:

- i) The designed filter has a cut-off frequencyHz
- ii) The designed filter has a roll-off factor dB/decade

Step 9

Open-ended Question / Can you answer this?

What will be the result if:

- 1) We repeat the frequency response readings for Passive High Pass Filter. How does it compare Active High Pass Filter
- 2) We sketch the frequency response of the passive and active second order HPF on the same graph sheet. What is the observation?