

ActiveLowPassFilter -- Overview



Dr. B Kanmani

Department Head,
Telecommunication Engineering

BMS College of Engineering (BMSCE),
Bangalore, India



OBJECTIVES:

At the end of performing this experiment, learners would be able to:

- Describe the concept of active Low Pass Butterworth Filter
- Obtain the roll-off factor and cutoff frequency of the filter designed
- Compare the designed cut-off frequency with the desired cut-off frequency
- Understand the working of $\mu A741$ IC (Op Amp)

EQUIPMENT:

- IC $\mu A741$
- Signal generator
- Resistors
- Capacitor
- +/- 15V DC Power Supply
- Digital Storage Oscilloscope & probes
- Connecting wires & Bread Board

DESIGN:

- Obtain the internal impedance R_S of the signal source
- Given cut-off frequency f Hz, assume suitable R , (greater than R_S),
- Calculate C using equation (5)
- Assume R_1 and compute R_2 using equation (6)

THEORY:

- Op - Amp is a DC-coupled high-gain electronic voltage amplifier with a differential input and a output.
- The $\mu A741$ device is a general-purpose operational amplifier featuring offset-voltage null capability
- The n poles of an n th order Butterworth filter lie on the left half of the s -plane, on a circle of radius unity (the poles have an angular

separation of π/n radians). The second order Butterworth filter has two poles p_1 and p_2 located on the left half of the s-plane as shown in the figure 1. Hence the transfer function of the filter with cut-off frequency $\omega_c = 1$ radians/second is given by

$$H(s) = \frac{1}{(s-p_1)(s-p_2)} \quad (1)$$

Where, $p_1 = (-0.707 + j0.707)$ and $p_2 = (-0.707 - j0.707)$

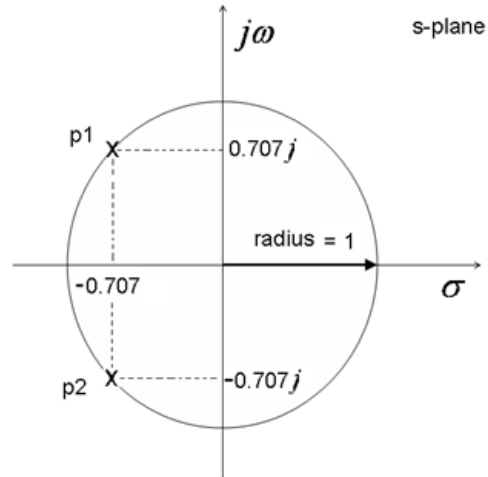


Figure 1: The two poles of the second order Butterworth low pass filter

Which is equivalent to

$$H(s) = \frac{1}{(s^2 + 1.414s + 1)} \quad (2)$$

To obtain the transfer function of a filter with cut-off ω_c radians/second, we replace s by s/ω_c , and we have,

$$H(s) = \frac{1}{((s/\omega_c)^2 + 1.414(s/\omega_c) + 1)} \quad (3)$$

The practical realization of the equation (3) is given by figure 2, has the transfer function

$$H_f(s) = \frac{(1/RC)}{(s^2 + ((3-A_f)/RC)s + (1/RC)^2)} \quad (4)$$

Comparing equations (3) and (4), we have the cut-off frequency as $\omega_c = 1/RC$ radians/second

or $f_c = \frac{1}{2\pi RC} \text{ Hz} \quad (5)$

with feedback gain A_f $A_f = \left(1 + \frac{R_2}{R_1}\right) = 1.586 \quad (6)$

Reference Reading:

- 1) Theory and application of Digital Signal Processing, by Lawrence R Rabin and Bernard Gold, Prentice Hall, Easter Economy Edition
- 2) Integrated Electronics, by Millman and Halkias, Tata McGraw-Hill

Acknowledgement


Mr. Shreenivas B for converting laboratory experiment to Tektronix courseware format

ActiveLowPassFilter -- Procedures

Step 1

Circuit setup:

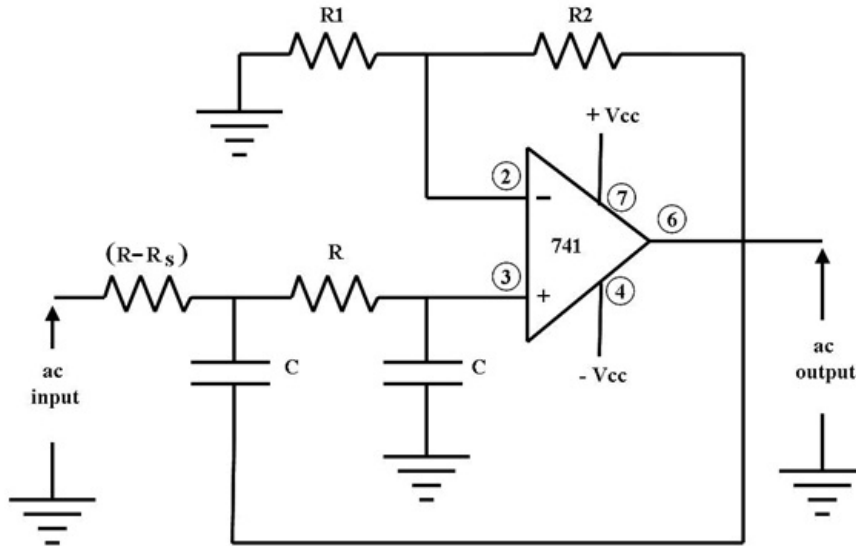Build the following circuit with given designed values



Second order low-pass active Butterworth filter

Step 2

- Use a signal generator to generate analog input . The analog input will be set to 1 Vpp Sine wave
- Turn on the supply of the circuit and enable signal generator that is feeding signal to the circuit.

Step 3

- Connect the DSO probe – CH1 at analog input (Sine wave), CH2 at output (pin # 6 of $\mu A741$ IC)
- Perform Autoset on DSO and capture the output signal.

Step 4

- Configure PEAK-to-PEAK measurement on the input and output signal.
- Observe and record the signal – input and output.


Step 5

Record the input and output peak-to-peak voltage for various input frequencies, and complete the table below

Frequency (Hz)	Vin(v)	Vout (v)	Gain (dB) = 20 log (Vout / Vin)
100 Hz			
200 Hz			
.....			
1KHz			
2KHz			
.....			
10KHz			
20KHz			
.....			
100KHz			
200KHz			
.....			
1MHz			


Step 6

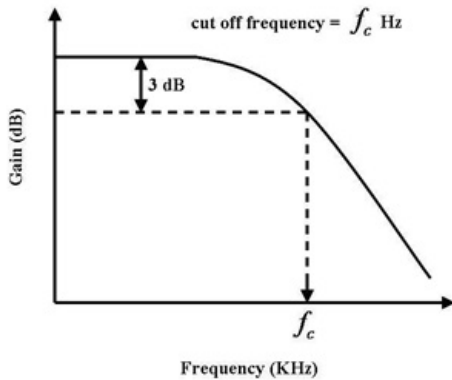Plot the frequency response of the designed filter (Plot of Frequency Vs. Gain on a semi-log sheet), and hence obtain the cut-off frequency



Step 7

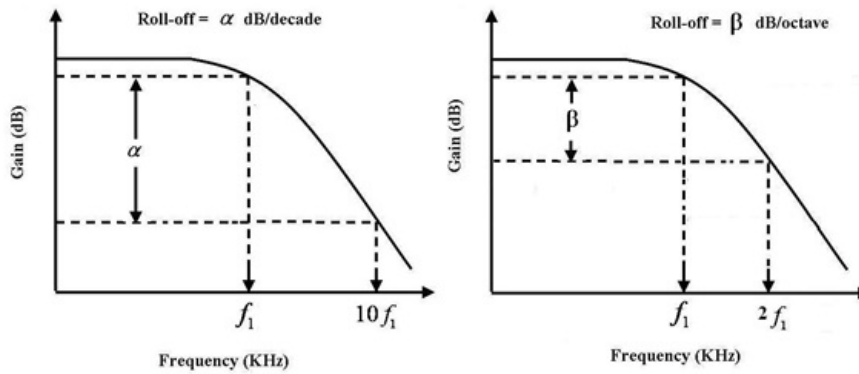Compute the Roll-off factor of the designed filter (The ideal value of roll-off factor is - 40dB/decade or -12dB/octave)



Step 8

Observations:

- i) The designed filter has a cut-off frequencyHz
- ii) The designed filter has a roll-off factor dB/decade

Step 9

Open-ended Question / Can you answer this?

What will be the result if:

- 1) We repeat the frequency response readings for Passive Low Pass Filter. How does it compare Active Low Pass Filter
- 2) We sketch the frequency response of the passive and active second order LPF on the same graph sheet. What is the observation?
- 3) We give a square wave equal to the designed cut-off frequency and record the output. Give reason if the output waveform is a sine wave.