

Activenarrowbandpass -- Overview



Dr. B Kanmani
Department Head,
Telecommunication Engineering

BMS College of Engineering (BMSCE),
Bangalore, India



OBJECTIVES:

At the end of performing this experiment, learners would be able to:

- Describe the concept of Resonant filter
- Obtain the Quality factor, Bandwidth and cutoff frequency of the filter designed
- Compare the designed cut-off frequency with the desired cut-off frequency
- Understand the working of $\mu A741$ IC (Op Amp)

EQUIPMENT:

- IC $\mu A741$
- Signal generator
- Resistors
- Capacitor
- Inductor
- +/- 15V DC Power Supply
- Digital Storage Oscilloscope & probes
- Connecting wires & Bread Board

DESIGN:

- Given second order active Bandpass filter with a centre frequency 5KHz, quality factor 10, and voltage gain 25
- Centre frequency

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \text{ Hz}$$

Choose L, compute C

- Given voltage gain A_o , choose R_1 and compute R_2

$$A_o = \left(1 + \frac{R_2}{R_1}\right)$$

- Given quality factor Q, compute resistor R, using

$$R = \frac{1}{Q} \sqrt{\frac{L}{C}}$$

THEORY:

- The $\mu A741$ device is a general-purpose operational amplifier featuring offset-voltage null capability
- Band pass filters have a frequency response as shown in figure 1. The difference between the two cut-off frequencies f_L (the lower cut-off) and f_H (the upper cut-off) is known as the bandwidth B_w .

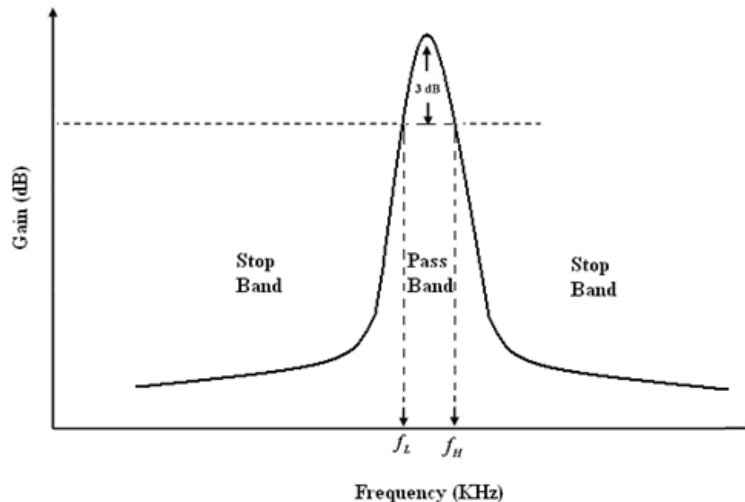


Figure 1: Frequency response of a narrow band-pass filter

- When the bandwidth B_w is small compared to either f_L or f_H the circuit is known as a resonant circuit with frequency response shown in figure 1.
- Resonant filters are characterized by the center or resonant frequency f_0 , and a high quality factor Q , where,

$$Q = f_0 / B_w \quad \text{and} \quad f_0 = \sqrt{f_L f_H}$$

Reference reading:

- 1) Theory and application of Digital Signal Processing, by Lawrence R Rabin and Bernard Gold, Prentice Hall, Eastern Economy Edition
- 2) Integrated Electronics, by Millman and Halkias, Tata McGraw-Hill

Acknowledgement

Mr. Shreenivas B for converting laboratory experiment to Tektronix courseware format

Active narrowbandpass -- Procedures

Step 1

Circuit setup:

Build the following circuit with designed values



- Use a signal generator to generate analog input . The analog input will be set to 1 Vpp Sine wave
- Turn on the supply of the circuit and enable signal generator that is feeding signal to the circuit.

- Connect the DSO probe – CH1 at analog input (Sine wave), CH2 at output (pin # 6 of μ A741 IC)
- Perform Autoset on DSO and capture the output signal.


- Configure PEAK-to-PEAK measurement on the input and output signal
- Observe and record the signal – input and output.

[illegible]

1MHz			

Step 6

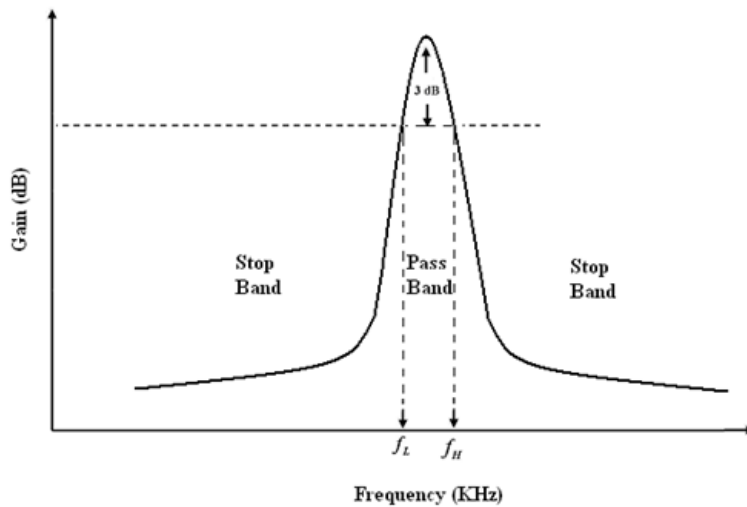Plot the frequency response of the designed filter (Plot of Frequency Vs. Gain on a semi-log sheet)



Step 7

Observations:

- The lower cut-off frequency f_L and the higher cut-off frequency f_H
- The bandwidth $Bw = f_H - f_L$
- The quality factor, $Q = f_0 / Bw$
- The voltage gain $A_0 = (V_0 / V_i)$, in the pass band of the filter

Step 8

Open-ended Question / Can you answer this?

If the designed parameters are not equal to the desired ones, give reasons.