

ASKwavefromGen -- Overview

Amplitude Shift Keying (ASK Modulation)



Dr. B Kanmani
Department Head,
Telecommunication Engineering

BMS College of Engineering (BMSCE),
Bangalore, India



OBJECTIVES:

At the end of performing this experiment, learners would be able to:

- Describe the concept of Modulation
- Obtain the Amplitude Shift Keying signal from given input
- Understand the working of LF398 IC (sample-and-hold circuit)

EQUIPMENT:

- IC LF398
- Signal generator
- Resistors – 47 k Ω
- +/- 15V DC Power Supply
- Digital Storage Oscilloscope & probes
- Connecting wires & Bread Board

THEORY:

- LF398 is a monolithic sample-and-hold circuit utilizing BI-FET technology for accurate fast acquisition of input signal.
- A sample and hold circuit is an analog device that samples (captures) the voltage of a continuously varying analog signal and holds (locks) its value at a constant level for a specified minimum period of time (hold time). They are typically used in analog-to-digital converters to eliminate variations in input signal that can corrupt the conversion process.
- Amplitude-shift keying (ASK) is the simplest form of digital modulation. ASK signal can be generated by product modulation that is, by multiplying the carrier with the rectangular waveform.

Reference reading:

B Kanmani, "Some applications of the combination: LM-741 and LF - 398", WASET CESSE 2009: International conference on Computer,

Acknowledgement


Mr. Shreenivas B for converting laboratory experiment to Tektronix courseware format

ASK waveform Gen -- Procedures

Step 1

Circuit setup:

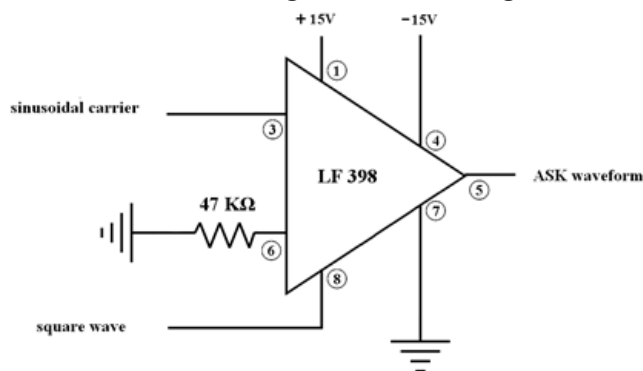Build the following circuit with given component values



Step 2


- Use a signal generator to generate Binary message data (square wave signal) input and carrier wave (sinusoidal signal). The binary data input will be set to 1 kHz square wave and carrier signal will be 15-20 kHz.
- Turn on the supply of the circuit and enable signal generator that is feeding signal to the circuit.
- Connect the DSO probe – CH1 at binary data input (pin # 8 of LF398 IC), CH2 at Sinusoidal carrier input (pin # 3 of the LF398 IC) and CH3 at output (pin # 5 of the LF398 IC).

Step 3

- Perform Autoset on DSO and capture the output signal.
- Configure PEAK-to-PEAK measurement on the input and output signal.
- Observe and record the signal – input and output.

Step 4

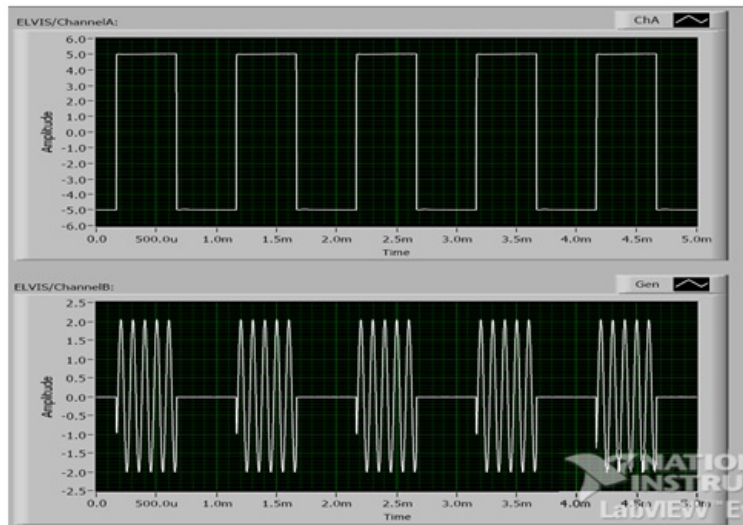Following figure shows the Binary message data and ASK waveform



Step 5

Observation:

The amplitude of the carrier is changed based on the input binary data being 1 or 0

Open-ended Question / Can you answer this?

What will be the effect on output waveform if:

- 1) Carrier input voltage is less than the binary data input voltage?
- 2) Carrier input voltage is more than the binary data input voltage?