

BFSK Generation -- Overview

Frequency Shift Keying (FSK Modulation)



Dr. B Kanmani
Department Head,
Telecommunication Engineering

BMS College of Engineering (BMSCE),
Bangalore, India



OBJECTIVES:

At the end of performing this experiment, learners would be able to:

- Describe the concept of modulation
- Obtain the Frequency shift keying (FSK) from given input
- Understand the working of LF398 IC (sample-and-hold circuit)

EQUIPMENT:

- IC LF398
- Signal generator
- Resistors – 47 k Ω
- +/- 15V DC Power Supply
- Digital Storage Oscilloscope & probes
- Connecting wires & Bread Board

THEORY:

- LF398 is a monolithic sample-and-hold circuit utilizing BI-FET technology for accurate fast acquisition of input signal.
- A sample and hold circuit is an analog device that samples (captures) the voltage of a continuously varying analog signal and holds (locks) its value at a constant level for a specified minimum period of time (hold time). They are typically used in analog-to-digital converters to eliminate variations in input signal that can corrupt the conversion process.
- In Frequency shift keying (FSK) , the waveforms $S_1(t) = A \cos W_1 t$ and $S_2(t) = A \cos W_2 t$ are used to convey binary digits 0 and 1 respectively.

Reference reading:

B Kanmani, "Some applications of the combination: LM-741 and LF - 398", WASET CESSE 2009: International conference on Computer,

Acknowledgement

Mr. Shreenivas B for converting laboratory experiment to Tektronix courseware format

BFSK Generation -- Procedures

Step 1

Circuit setup:

Build the following circuit with given component values

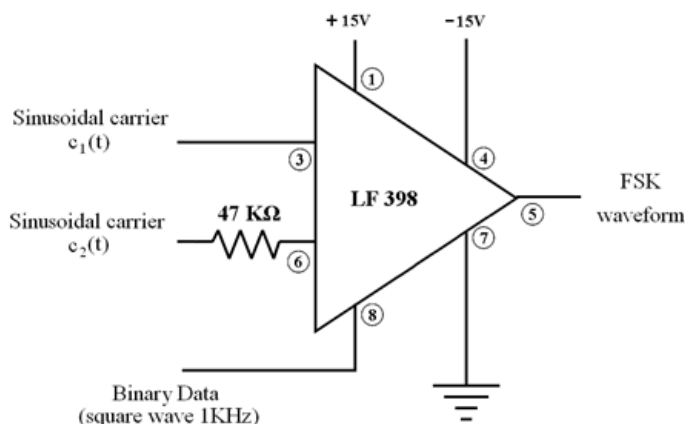


Figure 1: The circuit used to generate FSK output

Step 2

- Use a signal generator to generate Binary message data (square wave signal) input and two carrier wave (sinusoidal signal) $c_1(t)$ and $c_2(t)$. The binary data input will be set to 1 kHz square wave and carrier signal will be TWO different sinusoidal carriers of high frequency 15-20 kHz.

- Turn on the supply of the circuit and enable signal generator that is feeding signal to the circuit.

Step 3

- Connect the DSO probe – CH1 at binary data input (pin # 8 of LF398 IC), CH2 at Sinusoidal carrier input $c_1(t)$ (pin # 3 of the LF398 IC), CH3 at Sinusoidal carrier input $c_2(t)$ (pin # 6 of the LF398 IC) and CH4 at output (pin # 5 of the LF398 IC).

- Perform Autoset on DSO and capture the output signal.

Step 4

- Configure PEAK-to-PEAK measurement on the input and output signal.
- Observe and record the signal – input and output.

Step 5

The following figure has binary message signal with its corresponding BFSK output

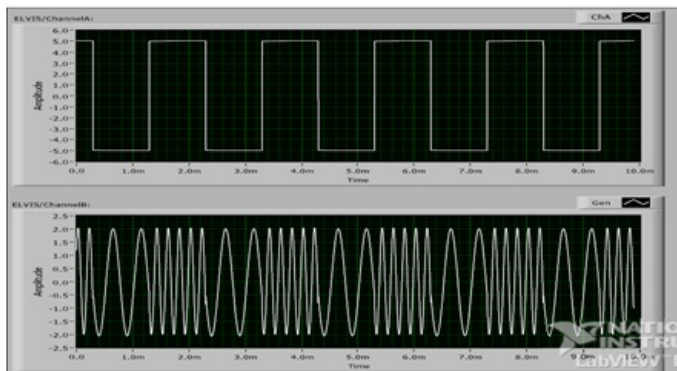


Figure 2: The binary message signal with its corresponding BFSK output

Step 6

Observation:

Symbols 1 and 0 are distinguished from each other by transmitting one of two sinusoidal waves that differ in frequency by a fixed amount

Open-ended Question / Can you answer this?

What will be the effect on output waveform if:

- 1) Two carrier signal have same frequency?
- 2) what are the voltage values for carrier and binary data signal ?