

DSBSC -- Overview

Double Sideband Suppressed Carrier Modulation



Dr. B Kanmani
Department Head,
Telecommunication Engineering
BMS College of Engineering (BMSCE),
Bangalore, India



OBJECTIVES:

At the end of performing this experiment, learners would be able to:

- Describe the concept of Double Sideband Suppressed Carrier modulation
- Obtain the DSBSC from given input
- Understand the working of LF398 IC (sample-and-hold circuit)
- Understand the working of μ A 741 IC

EQUIPMENT:

- IC LF398
- IC μ A 741
- Signal generator
- Resistors – 47 k Ω , 1 k Ω
- Capacitor – 0.01 μ F
- Decade inductance box
- +/- 15V DC Power Supply
- Digital Storage Oscilloscope & probes
- Connecting wires & Bread Board

DESIGN OF BPF :

$$f = 1/(2\pi\sqrt{LC})$$

$$f = 30\text{kHz}$$

$$L = ?$$

$$\text{let } C = 0.01\mu\text{F}$$

$$L = 2.18\text{mH}$$

THEORY:

- LF398 is a monolithic sample-and-hold circuit utilizing BI-FET technology for accurate fast acquisition of input signal.
- A sample and hold circuit is an analog device that samples (captures) the voltage of a continuously varying analog signal and holds (locks) its value at a constant level for a specified minimum period of time (hold time). They are typically used in analog-to-

digital converters to eliminate variations in input signal that can corrupt the conversion process.

- DSBSC Modulation carrier component is suppressed from the modulated wave resulting in Double Sideband Suppressed Carrier modulation

Reference reading:

B Kanmani, "Some applications of the combination: LM-741 and LF - 398", WASET CESSE 2009: International conference on Computer, Electrical and Systems science and Engineering, Rome, 28th-30th April, Italy, 2009. Volume 52, April 2009, ISSN: 2070-3724, pages 335-340.

Acknowledgement


Mr. Shreenivas B for converting laboratory experiment to Tektronix courseware format

DSBSC -- Procedures

Step 1

Circuit setup:

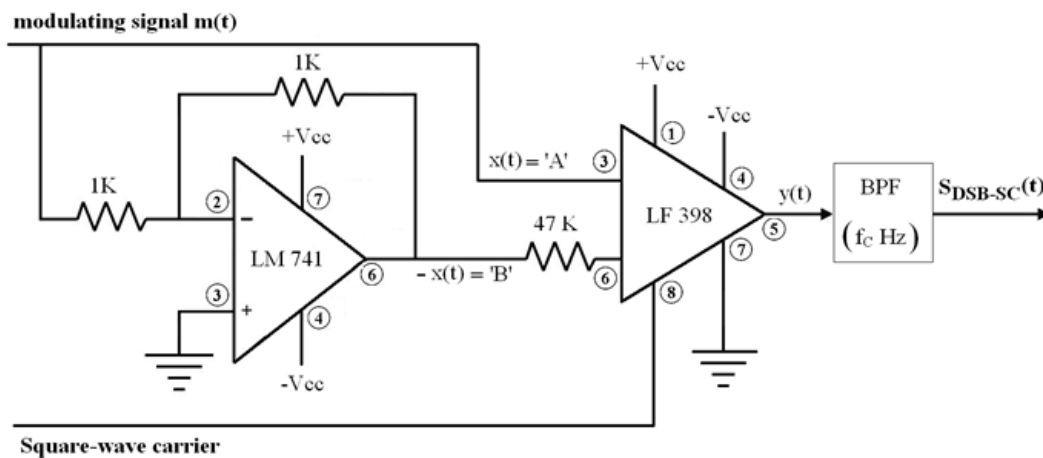Build the following circuit with given component values



Step 2

- Use a signal generator to generate modulating signal $m(t)$ (sine wave of 5kHz for example) and carrier frequency (square wave signal).
- Design the BPF for the carrier frequency of 30kHz
- Turn on the supply of the circuit and enable signal generator that is feeding signal to the circuit.
- Tune the circuit, by varying the carrier frequency so that output of the BPF is maximum

- The modulating signal will be set to 5 kHz Sine wave


Step 3

- Connect the DSO probe – CH1 at modulating input (pin # 3 of LF398 IC), CH2 at carrier input (pin # 8 of LF398 IC), CH3 at (pin # 6 of μ A 741 IC) and CH4 at output
- Perform Autoset on DSO and capture the output signal.

Step 4

- Configure PEAK-to-PEAK measurement on the input and output signal.
- Observe – input and output on DSO and record the signal

Step 5

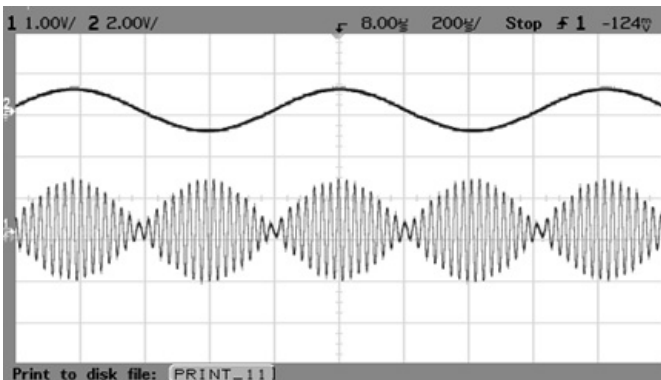

Step 6

Observation:

- Op-Amp output will be 180degree phase shifted

Open-ended Question / Can you answer this?

What will be the effect on output waveform if:

- 1) Capacitor value is changed from $0.01\mu\text{F}$ to $0.1\mu\text{F}$?
- 2) Modulating signal dc-offset is given ?