

Linearity -- Overview

System Linearity



Dr. B Kanmani
Department Head,
Telecommunication Engineering

BMS College of Engineering (BMSCE),
Bangalore, India



OBJECTIVES:

At the end of performing this experiment, learners would be able to:

- Understand the linearity of the given system
- Satisfying the Superposition theorem
- Test the RC LPF for linearity.

EQUIPMENT:

- Signal generator
- Resistors – 1 k Ω
- Capacitor – 1 μ F
- Digital Storage Oscilloscope & probes
- Connecting wires & Bread Board

THEORY:

Two quantities that are directly proportional to each other, such as voltage and current in a simple DC circuit

Acknowledgement


Mr. Shreenivas B for converting laboratory experiment to Tektronix courseware format

Linearity -- Procedures

Step 1

Circuit setup:

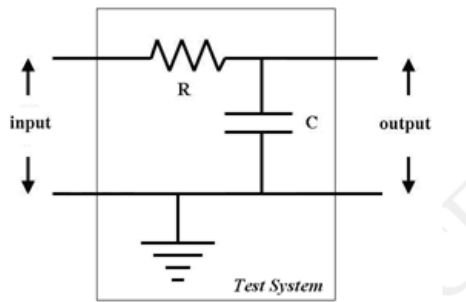
Build the following circuit with given component values



Step 2

- Choose $R = 1\text{ K}\Omega$ and $C = 1\mu\text{F}$ (some typical value)
- Use a signal generator to generate sine wave of 2Vpp (input-I) and square wave of 2Vpp (input- II)
- Observe the corresponding output

Step 3

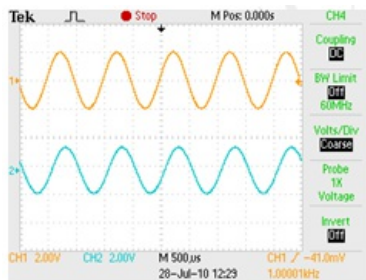


input - I

output - I

Step 4

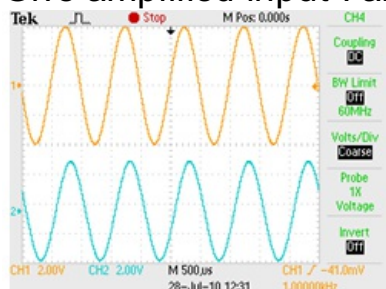Give amplified input-I and observe the corresponding output




amplified input - I

amplified output - I

Step 5

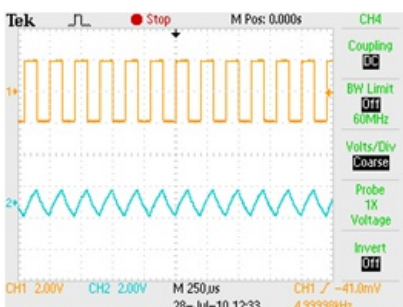Give input-II and observe the corresponding output




input - II

output - II

Step 6

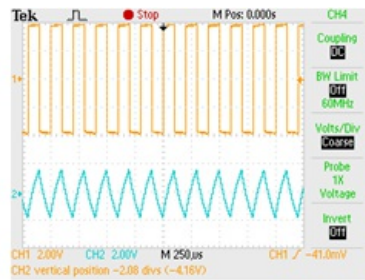Give amplified input-II and observe the corresponding output




amplified input - II

amplified output - II

Step 7

Obtain the SUM of the two inputs

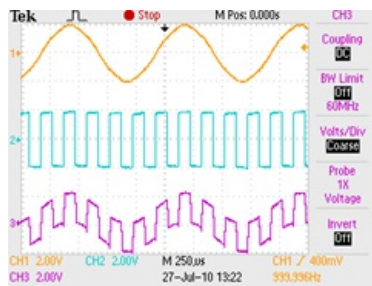


input - I

input - II

$(\text{input - I}) + (\text{input - II})$

Step 8

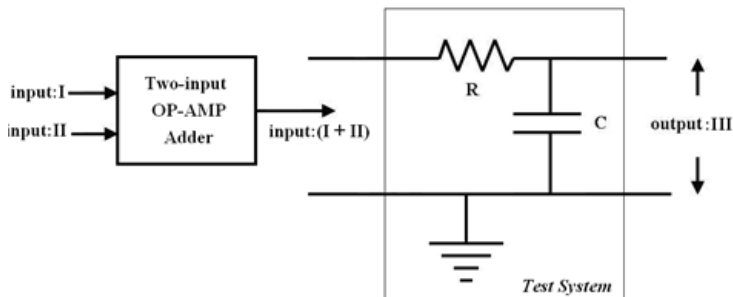Give the SUM of the two inputs and observe the corresponding output



Step 9




$(\text{input : I}) + (\text{input : II})$


corresponding output

Step 10

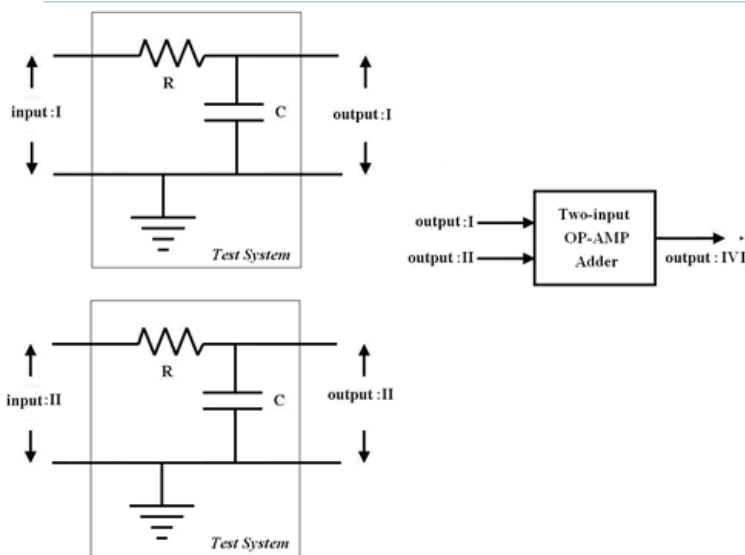Connect another similar circuit, and obtain the SUM of the two outputs



Step 11

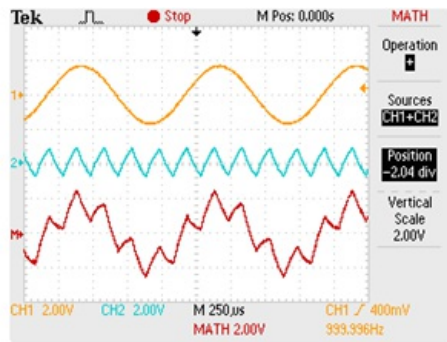

output : I

output : II

$(\text{output : I}) + (\text{output : II})$

Step 12

Observation

- 1) Results of Steps III and V satisfy Amplitude scaling property
- 2) Results of Steps VII and VIII prove superposition theorem

Open-ended Question / Can you answer this?

What will be the effect on output waveform if:

- 1) For a linear time invariant system when the input is sinusoidal, the corresponding output is of same _____ with change in _____ and some _____
- 2) Different circuit, involving RL or RC or LC or RLC