

Notchfilters -- Overview



Dr. B Kanmani
Department Head,
Telecommunication Engineering

BMS College of Engineering (BMSCE),
Bangalore, India



OBJECTIVES:

At the end of performing this experiment, learners would be able to:

- Describe the concept of Narrow band filter
- Obtain the Rejection Band and cutoff frequency of the filter designed
- Compare the designed cut-off frequency with the desired cut-off frequency
- Understand the working of $\mu A741$ IC (Op Amp)

EQUIPMENT:

- IC $\mu A741$
- Signal generator
- Resistors
- Capacitor
- +/- 15V DC Power Supply
- Digital Storage Oscilloscope & probes
- Connecting wires & Bread Board

DESIGN:

The rejection frequency f_R is given by

$$f_R = \frac{1}{2\pi RC}$$

Assuming capacitor, the resistance can be computed. Better accuracy is obtained

by using two resistors and two capacitors of value R and C, instead of single resistor and capacitor of values R/2 and capacitor 2C.

Given frequency 1KHz, Let C = 0.1 μ F

$$f = 1/2\pi RC$$

$$R = 1.59k\Omega$$

THEORY:

- The $\mu A741$ device is a general-purpose operational amplifier

featuring offset-voltage null capability

- Narrow band reject filters are also known as Notch filters. They are designed to reject a single frequency.

Reference reading:

- 1) Theory and application of Digital Signal Processing, by Lawrence R Rabine and Bernard Gold, Prentice Hall, Easter Economy Edition
- 2) Integrated Electronics, by Millman and Halkias, Tata McGraw-Hill

Acknowledgement


Mr.Shreenivas B for converting laboratory experiment to Tektronix courseware format

Notchfilters -- Procedures

Step 1

Circuit setup:

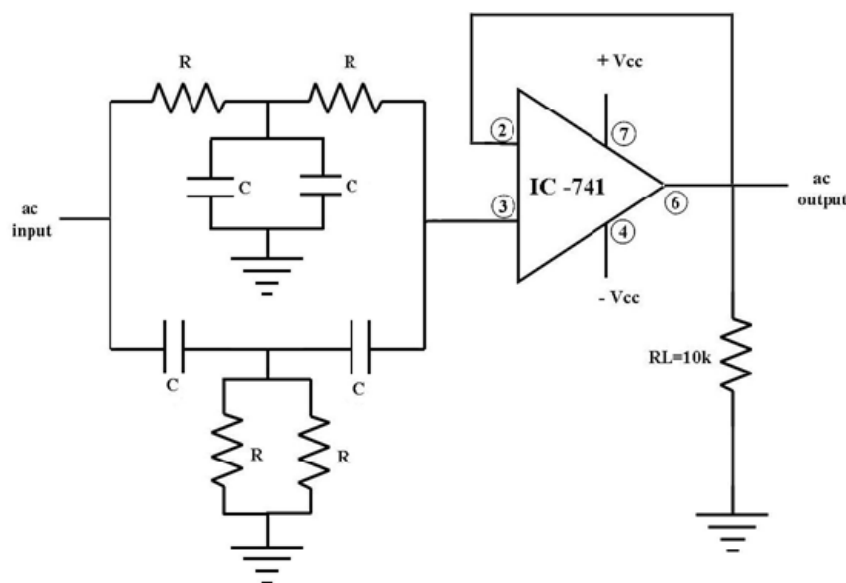Build the following circuit with designed values



Step 2

- Use a signal generator to generate analog input . The analog input will be set to 1 Vpp Sine wave
- Turn on the supply of the circuit and enable signal generator that is feeding signal to the circuit.

Step 3

- Connect the DSO probe – CH1 at analog input (Sine wave), CH2 at output (pin # 6 of $\mu A741$ IC)

- Perform Autoset on DSO and capture the output signal.

Step 4

- Configure PEAK-to-PEAK measurement on the input and output signal
- Observe and record the signal – input and output.


Step 5

Record the input and output peak-to-peak voltage for various input frequencies, and complete the table below.

Frequency (Hz)	Vin(v)	Vout(v)	Gain (dB) = $20\log(V_{out}/V_{in})$

Step 6

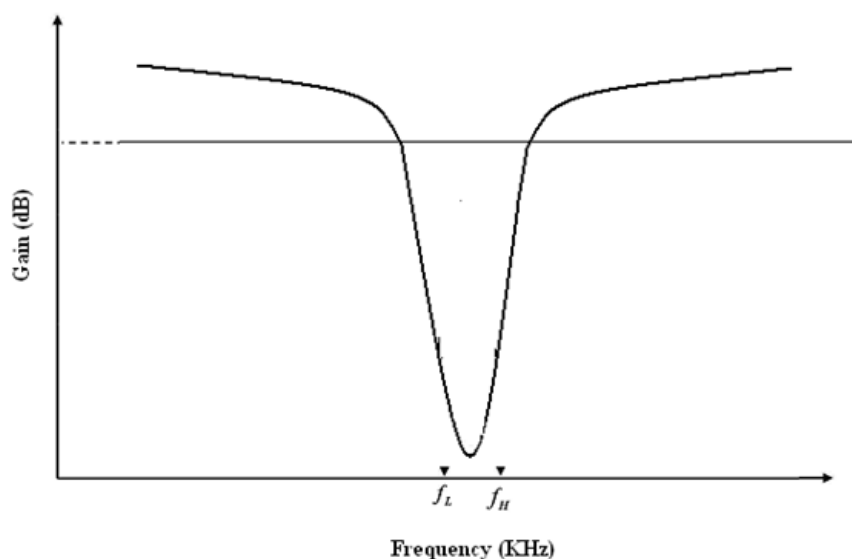Plot the frequency response of the designed filter (Plot of Frequency Vs. Gain on a semi-log sheet)



Step 7

Observation:

- 1) The lower cut-off frequency f_L and the higher cut-off frequency

Fh .

2) The bandwidth $BW = F_h - F_l$

Step 8

Open-ended Question / Can you answer this?

If the designed parameters are not equal to the desired ones, give reasons.