OpampIntegrator -- Overview



Mukesh Soni Product Marketing Manager Basic Scopes Product Line Tektronix

Tektronix

OBJECTIVES

After performing this lab exercise, learner will be able to:

- Design & build Opamp Integrator circuit
- Use 2231A power supply to provide bipoal DC voltage (+/- 10V) to the OPAMP circuit
- Use digital oscilloscope's trigger to capture and display the signal
- Establish relationship between input and output signal

EQUIPMENT

To carry out this experiment, you will need:

- TBS1KB Digital Oscilloscope from Tektronix
- Voltage probe (provided with oscilloscope) / BNC cables
- Circuit components
 - Opamp (741 IC or equipvalent),
 - Resistor and
 - capacitor
- Breadboard and connecting wires
- Regulated DC supply 0-30V DC (Keithley 2231A)
- Signal /Function generator (AFG3000 from Tektronix)

THEORY

Key concepts:

- An opamp is a high-gain differential amplifier with very high input impedance.
- OPAMP integrator circuit produces output proportional to integral of its input.

Integrator



• If a square wave is input to Integrator circuit, the output will be triangular wave



 2231A power supply has 3 independent channels for DC power.
 CH1 and CH2 can be combined in series to provide bipolar (+/-) DC voltage needed for Opamp circuit.

OpampIntegrator -- Procedures

Step 1

DUT / CIRCUIT SETUP

• Build the circuit as shown below:



Step 2

AFG / SIGNAL GENERATOR SETUP

- Switch on the AFG signal to provide input to Diode circuit
- Set Square wave of 2Vpk-pk, 1kHz on signal generator / AFG

Step 3

POWER SUPPLY SETUP

We will have to use 2 channels of DC power supply, connected in series:

- 1. Select CH1
- 2. Set voltage as 2V
- 3. Select CH2
- 4. Set voltage to be 2V
- 5. Press MENU button on the front panel and select Combine Ch1
 + Ch2
- 6. Push the down arrow key to select the option V1+V2 Series
- 7. Ensure the connections as below (for Vcc and Vee bipolar supply to Opamp circuit)



Step 4

OSCILLOSCOPE PROBING

- Power ON the oscilloscope
- Connect the Channel 1 probe of the oscilloscope to Vin
- Connect the Channel 2 probe to Vout
- Acquire the signal(s) from circuit on oscilloscope

Step 5

• Do the Autoset on the scope to efficiently capture and view the signal

• If AUTOSET feature is not enabled, then manually set the horizontal and vertical scale, and trigger condition to view 3-4 cycles of waveform without any clipping.

Step 6

ADDING OSCILLOSCOPE MEASUREMENTS

• Go to measurement menu by pressing **MEASURE** button on the scope front panel

• Press CH1 and select MAXIMUM and MINIMUM measurement using Multi-Purpose Knob (MPK) button

Add similar measurements for CH2

• You can navigate through the measurement list by rotating the MPK knob and select a measurement by pressing it

Step 7

• Record the measurement values and waveform / screenshot

• Verify the measurement parameters against designed (calculated based on circuit components)

Step 8

CAN YOU ANSWER THIS?

• What will be the output of the integrator circuit if the input is a sine wave?