

# PrecisionFWRectifier -- Overview

**Prof. S.Sundar**

AP(Sr)

Electronics Engineering  
Vellore Institute Of Technology

## Objectives:

To design full wave precision rectifiers using op-amps.

## Pre lab questions:


1. What is the difference between an ordinary rectifier and a precision rectifier using op-amps?
2. Identify the diode which will be ON during the positive half cycle in the half wave rectifier circuit below.
3. Identify the diode/diodes which will be ON during the positive half cycle in the full wave rectifier circuit below.

## Components & Equipments required:


1. Operational amplifier -  $\mu A 741$
2. Resistors
3. Diodes
4. Signal generator
5. CRO
6. Bread board
7. Power supply
8. Connecting wires

## Half wave rectifier:

## Circuit and Design:

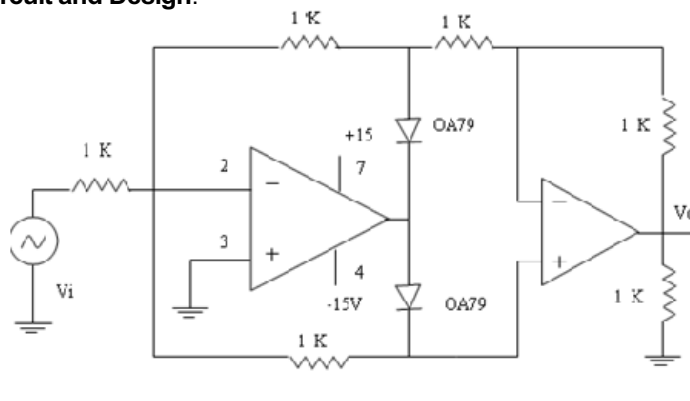


## Model Graph:

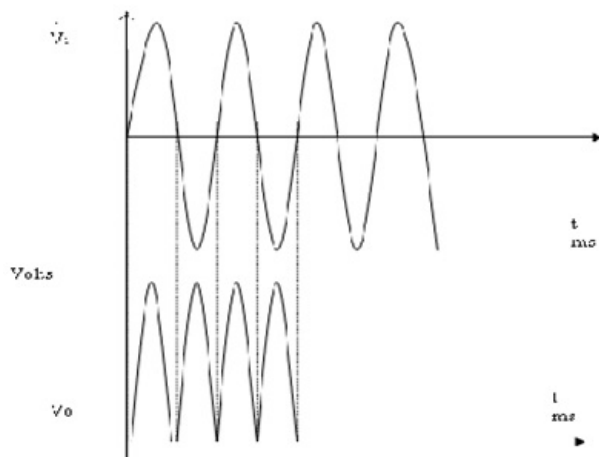

# PrecisionFWRectifier -- Procedures

## Step 1

Connect the circuit as shown below.

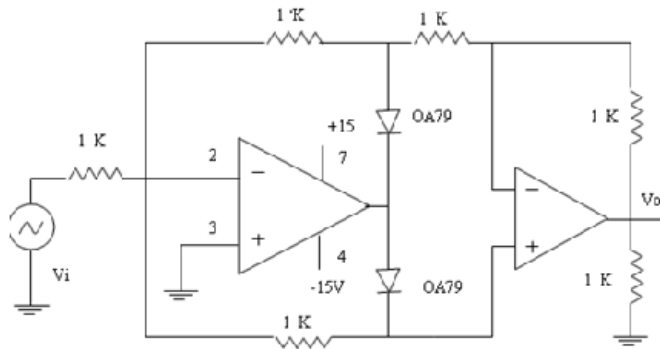


## Step 2

Apply a small signal say 500mV, 1 kHz sine signal as  $V_i$
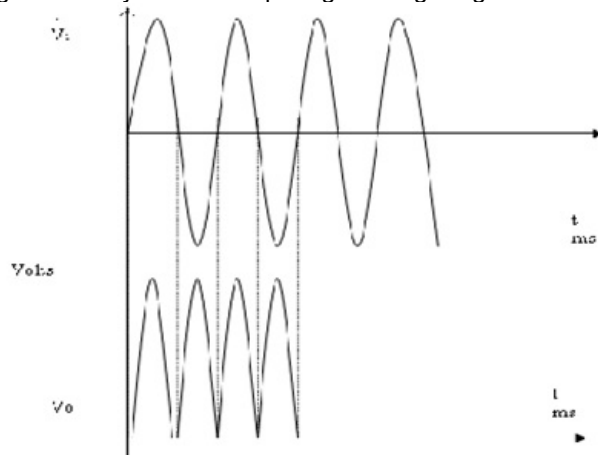
## Step 3

Observe the output  $V_o$  and input  $V_i$  simultaneously in the two channels of CRO. Verify if both positive and negative half cycles of the input signal are getting rectified as shown below.



## Step 4

Plot your observations in a graph sheet.

## Step 5

### Post lab questions:

1. Apply triangular / square wave as inputs to the rectifier circuits and observe the outputs.
2. Does your full wave rectifier rectify ac signals of amplitude less than 1 volt?

## Step 6

Inference/Result: