


PulsAmplitudeMod_PAM -- Overview

Dr. Alex Noel Joseph Raj Professor Embedded Division	Ms. Vijayalakshmi GV Research Scholar	
School of Electronics (SENSE)		
Vellore Institute of Technology (VIT), Vellore, Tamilnadu (India)		

Objectives:

At the end of performing this experiment, learners would be able to:

- Describe the concept of Pulse Amplitude Modulation
- Understand the working of PAM under different sampling conditions
- Identify the concept of envelope detection
- Demodulate the PAM signal

Equipment:

- Transistor SL100
- Signal generator
- Resistors
- Capacitor
- Digital Storage Oscilloscope & probes
- Connecting wires & Bread Board

Theory:

- Pulse Amplitude Modulation is a form of signal modulation where the message information is encoded in the amplitude of a series of signal pulses. The output is a series of pulses, the amplitude of which vary in proportion to the modulating signal. The samples are taken at regular interval of time.

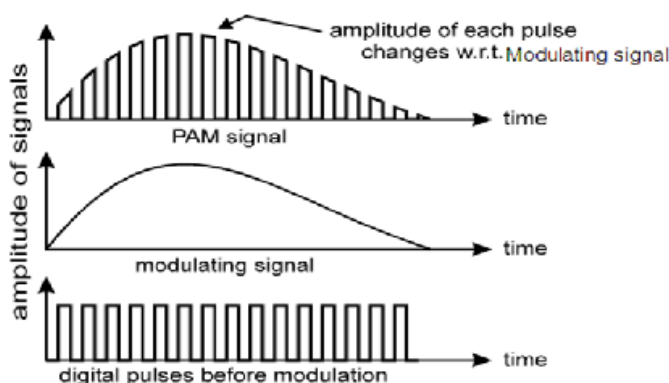


Figure (1): Pulse Amplitude Modulation

- Demodulation is performed by detecting the amplitude level of

the carrier at every symbol period. If enough samples are taken, a reasonable approximation of the signal being sampled can be constructed at the receiving end.

Design:

Given the specifications

- $I_c = \text{----- mA}$,
- $h_{fe} = \text{-----}$,
- $V_{CE \text{ sat}} = \text{-----V}$,
- $V_{BE \text{ sat}} = \text{-----V}$ and
- $f_m = \text{-----Hz}$

Design the biasing circuit

- To find R_c
 - $V_m(t) = I_c \times R_c + V_{CE \text{ sat}}$ Where $V_m(t)$ = Amplitude of the modulating signal

$$R_c = \frac{V_m(t) + \text{DC shift} - V_{CE \text{ sat}}}{I_c}$$

- To find R_B

$$V_c(t) = I_B \times R_B + V_{BE \text{ sat}}$$

$V_c(t)$ = Amplitude of the carrier signal,

$$R_B = \frac{V_c(t) - V_{BE \text{ sat}}}{I_B}$$

where $I_B = I_c / h_{fe}$

- To design Filter/ envelope detector
 - Cut off frequency of the filter $f_o \gg f_m$, choose $f_o = \text{----- Hz}$
where $f_o = 1 / 2\pi RC$
 - Assume $C = \text{-----}\mu\text{F}$ and
 - find R , which is given by $R = 1 / 2\pi f_o C$

Reference reading:


- Introduction to Analog and Digital Communication by Simon Haykin, 2e, Wiley.

PulsAmplitudeMod_PAM -- Procedures

Step 1

Circuit setup:

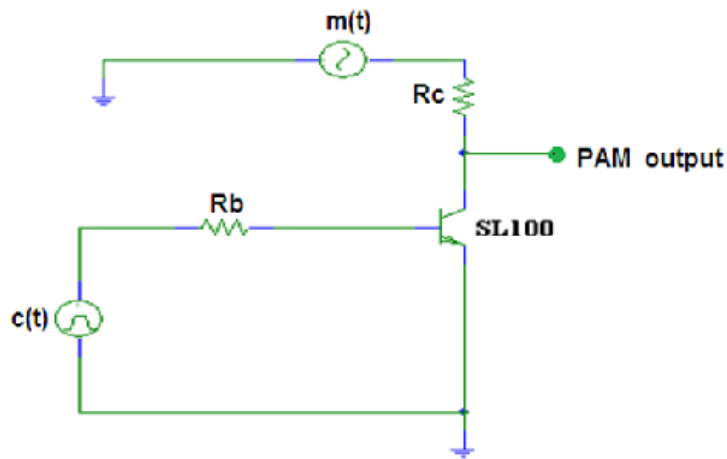Build the following circuit to obtain the PAM signal



Circuit diagram of modulator

Step 2

Use a signal generator to generate:

- A sine wave modulating signal $m(t)$ of
 - frequency $f_m(t) = 100 \text{ Hz}$ and
 - amplitude $V_m(t) = 5\text{V}$ (peak to peak) and a 3V DC Shift
- Square wave carrier signal $c(t)$ of
 - frequency $f_c(t) = 5\text{K Hz}$ with
 - amplitude $V_c(t) = 2\text{V}$ (peak to peak)

Step 3

- Apply the modulating signal $m(t)$ and the carrier signal $c(t)$ to the circuit as shown in Step1


Step 4

- Connect the DSO probe – CH1 to the modulating signal and CH2 to the output and observe the PAM signal (variation in the amplitude of carrier wave with respect to the modulating signal).
- Take screenshot

Step 5

Circuit setup:

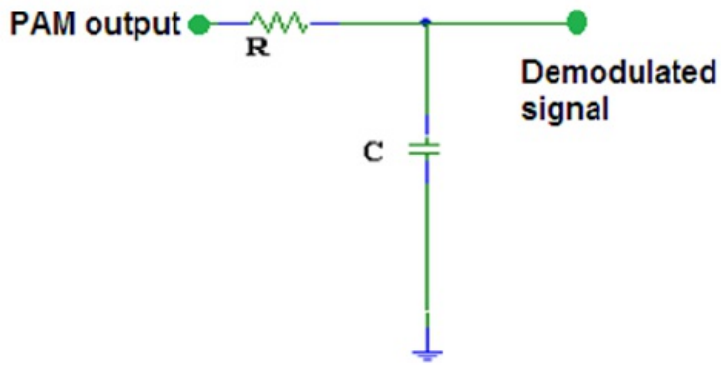Build the demodulator circuit with the designed values



Step 6

- Apply the PAM output as input to the Demodulator circuit
- Connect the DSO probe – CH1 to the modulating signal and CH2 to the output of the demodulator circuit and observe the demodulated signal (take screenshot)

Step 7

- Repeat the Steps from 2 through 7 for
 - $f_c = 2f_m$
 - $f_c < 2f_m$
 - $f_c > 2f_m$

Step 8

Open-ended Question / Can you answer this?

What will be the result if:

- 1) We change the transistor to SK100?
- 2) We connect a diode (forward or reverse biased) before resistor in series with it in the demodulator circuit ?