

Resfilterwithoutinducto -- Overview

Resonant Filter (without inductor)



Dr. B Kanmani
Department Head,
Telecommunication Engineering
BMS College of Engineering (BMSCE),
Bangalore, India



OBJECTIVES:

At the end of performing this experiment, learners would be able to:

- Describe the concept of Resonant filter
- Obtain the Quality factor, Bandwidth and cutoff frequency of the filter designed
- Compare the designed cut-off frequency with the desired cut-off frequency
- Understand the working of $\mu A741$ IC (Op Amp)

EQUIPMENT:

- IC $\mu A741$
- Signal generator
- Resistors
- Capacitor
- +/- 15V DC Power Supply
- Digital Storage Oscilloscope & probes
- Connecting wires & Bread Board

DESIGN:

- Given second order active Bandpass filter with a centre frequency 5KHz, quality factor 10, and voltage gain 25

Given the following parameters:

voltage gain $A_0 = (V_o/V_i)$,

the center frequency ω_0 , with $f_0 = \sqrt{f_L f_H}$,

and the quality factor, $Q = f_0/Bw$, where $Bw = f_H - f_L$

- Compute R_s , the internal resistance of the signal source
- Choose R_1 , higher than R_s
- Obtain C_1 from the following equation
 $-R_1 C_1 = Q / (\omega_0 A_0)$

- Assume $C_1 = C_2$

- Compute R_3 from,

$$R_3 \frac{C_1 C_2}{C_1 + C_2} = \frac{Q}{\omega_0}$$

- Compute R_2 from

$$(R_1 \parallel R_2) R_3 C_1 C_2 = \frac{1}{\omega_0^2}$$

THEORY:

- The $\mu A741$ device is a general-purpose operational amplifier featuring offset-voltage null capability
- Band pass filters have a frequency response as shown in figure 1. The difference between the two cut-off frequencies f_L (the lower cut-off) and f_H (the upper cut-off) is known as the bandwidth B_w .

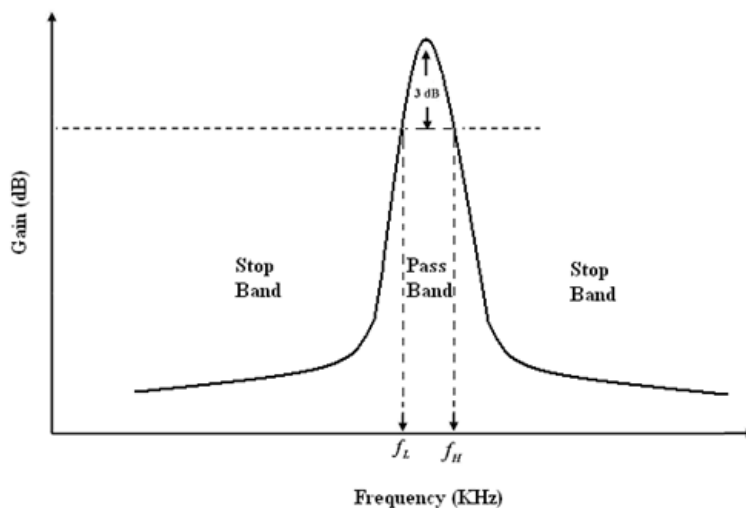


Figure 1: Frequency response of a narrow band-pass filter

- When the bandwidth B_w is small compared to either f_L or f_H the circuit is known as a resonant circuit with frequency response shown in figure 1.

Reference reading:

- 1) Theory and application of Digital Signal Processing, by Lawrence R Rabin and Bernard Gold, Prentice Hall, Easter Economy Edition
- 2) Integrated Electronics, by Millman and Halkias, Tata McGraw-Hill

Acknowledgement


Mr. Shreenivas B for converting laboratory experiment to Tektronix courseware format

Resfiltwithoutinducto -- Procedures

Step 1

Circuit setup:

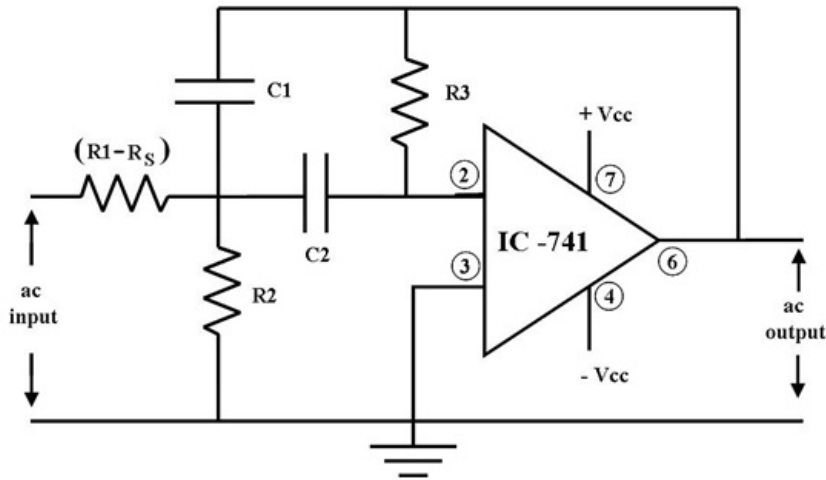Build the following circuit with designed values



Active second order band-pass filter without inductor

Step 2

- Use a signal generator to generate analog input . The analog input will be set to 1 Vpp Sine wave
- Turn on the supply of the circuit and enable signal generator that is feeding signal to the circuit.

Step 3

- Connect the DSO probe – CH1 at analog input (Sine wave), CH2 at output (pin # 6 of $\mu A741$ IC)
- Perform Autoset on DSO and capture the output signal.

Step 4

- Configure PEAK-to-PEAK measurement on the input and output signal
- Observe and record the signal – input and output.

Step 5

Record the input and output peak-to-peak voltage for various input frequencies, and complete the table below.

Frequency	$V_{in}(V)$	$V_{out}(V)$	Gain = $20 \log$

