

Sallen-Key_Low_Pass_Filter -- Overview



Mukesh Soni
Researcher / PhD Student
Mechanical Engineering Department
The University of Melbourne



Sallen-Key Low Pass Filter

Objectives:

After performing this lab exercise, learner will be able to:

- Understand & analyze working of Sallen-Key topology of active filters
- Design & build a Sallen-Key low pass filter using opamp
- Establish relationship between input and output signal - prepare a Bode plot for the filter circuit
- Practice working with measuring equipment and laboratory tools like digital oscilloscope, signal generator, multimeter and power supply
- Use digital oscilloscope to debug/analyze the circuit

Equipment:

To perform this lab experiment, learner will need:

- Digital Storage Oscilloscope (TBS1000B-Edu from Tektronix or any equivalent)
- Power Supply (2231A-30-3 Power Supply from Keithley or any equivalent power supply capable of supplying +/- 10V DC)
- Signal generator (AFG1000 from Tektronix or equivalent) for providing AC input to circuit
- Multimeter
- Electronic Components
 - Opamp 741 / TL082 or equivalent - as single IC or as part of any analog circuit kit (like ASLK board from TI)
 - Resistor (2 x 1K ohms)
 - Capacitor (2 x 0.1 uF)
- BNC cables
- Breadboard and connecting wires



Theory / Key Concepts:


Before performing this lab experiment, it is important to learn following concepts:

- An opamp is a high-gain differential amplifier with very high input impedance. Very high open-loop gain allow for creating amplifiers with stable gain using feedback.
- A low pass filter is an electronic circuit that passes signals with a frequency lower than a certain value and attenuates signals of higher frequencies.
 - The 'certain' frequency after which the attenuation starts is called as 'cut-off frequency' of the filter.
 - Range of frequencies below cut-off frequency is called pass-band and higher frequency ranges are called stop band.
- At cut-off frequency, the signal amplitude is 0.707 times of its value in the passband i.e., the signal level is 3dB below the passband value.
- Professors R.P. Sallen and E.L. Key described a new filter topology in 1955, which was named after them, the Sallen-Key filters.
- An active Sallen-Key filter can be cascaded easily to make higher order filters. The opamp provides the buffering buffering between cascaded stages.
- Sallen-Key filter gives the flexibility of modifying the filter characteristics (cut-off frequency and Q) using R, C values and amplifier gain. This makes filter design easy.
- Low pass filter is used for eliminating high-frequency noise from the system.

Circuit Design:

Learner can use the theoretical design rules to calculate the circuit component values:

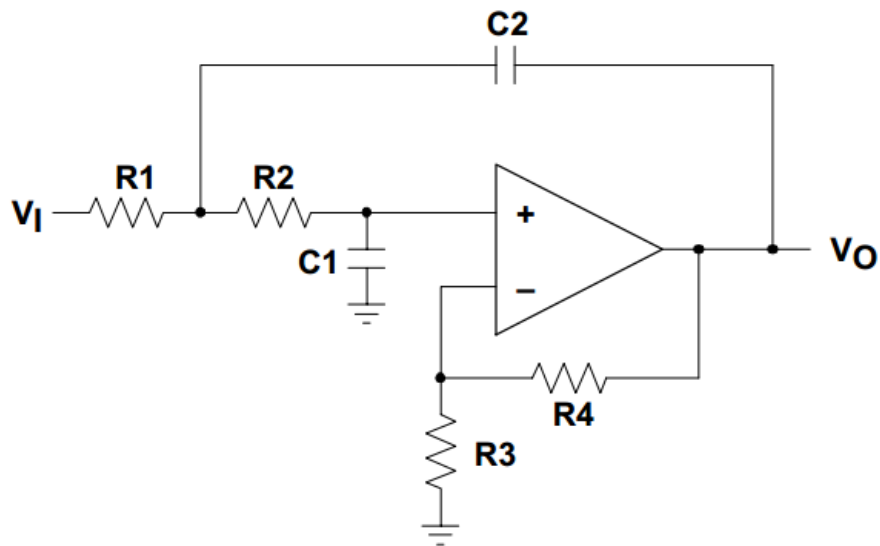- A generic Sallen-Key low pass filter circuit is shown below with filter parameters:



Where:

- $K = \text{amplifier gain} = 1 + (R4 / R3)$
- Transfer function = V_0/V_i

$$= \frac{K}{s^2(R1R2C1C2) + s(R1C1 + R2C1 + R1C2(1 - K)) + 1}$$


- Cut-off frequency =

$$f_c = \frac{1}{2\pi \sqrt{R1R2C1C2}}$$

and

$$Q = \frac{\sqrt{R1R2C1C2}}{R1C1 + R2C1 + R1C2(1 - K)}$$

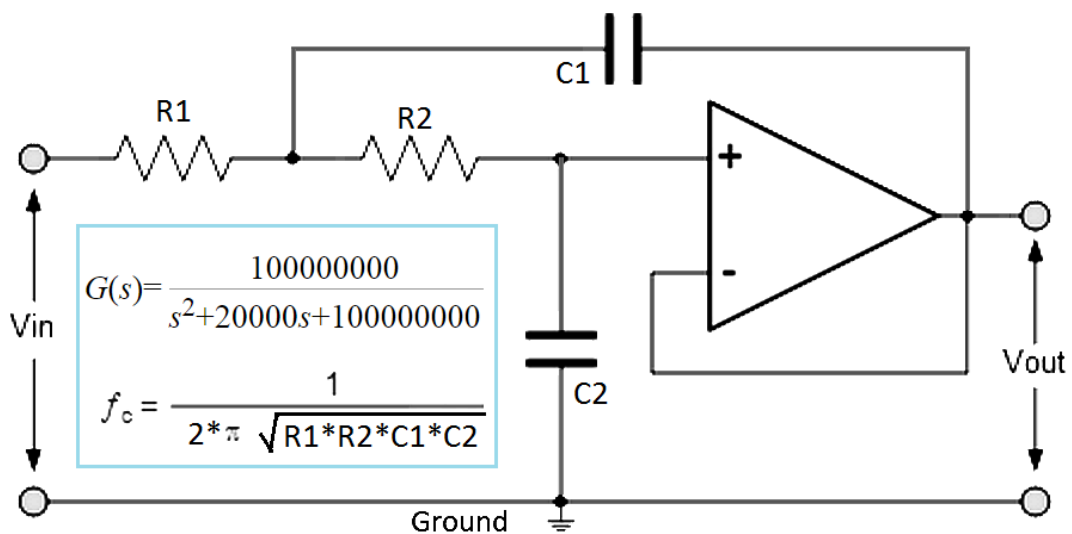- We can simplify the filter design by choosing $R1 = R2 = R = 1k$ Ohms and $C1 = C2 = C = 0.1\mu F$. The opamp gain is kept unity ($R4 = 0$ and $R3 = \text{infinity}$).



- This makes
 - Amplifier gain $K = 1$
 -

- With the given R and C values, the cut-off frequency will be 1592 Hz, $Q = 1/2$ and K (opamp amplifier gain) = 1

Sallen-Key_Low_Pass_Filter -- Procedures

Step 1

Check Your Understanding:


Before performing this lab experiment, learners can check their understanding of key concepts by answering these?

- What will be the slope of magnitude response in the stop band of a Sallen-Key low-pass filter?
 - -20dB / decade
 - 0 dB / decade
 - -40dB / decade
 - +20dB / decade
- How will the phase responses for Sallen-Key low pass filter vary with frequency of input signal?
 - Phase will vary from 0 to 90 degrees as frequency goes low to high
 - Phase will vary from 0 to -90 degrees as frequency goes low to high
 - Phase will vary from 0 to -180 degrees as frequency goes low to high
 - Phase will vary from 180 to 0 degrees as frequency goes low to high
- The response of the filter circuit will not produce any overshoot or oscillation for:
 - $Q = 1$
 - $Q = 0.5$
 - $Q < 0.5$
 - $Q = \text{infinity}$

Step 2

Circuit diagram / Connection Details

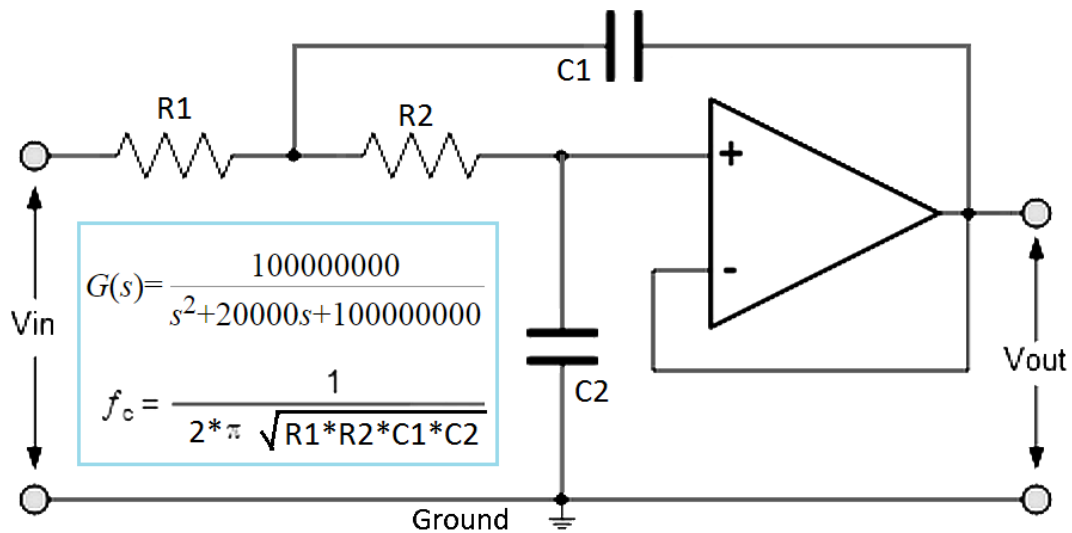
- Using the jumper / connecting wires prepare the circuit as shown below - Choose $C1 = C2 = 0.1\mu\text{F}$ & $R1 = R2 = 1\text{k ohm}$.
- When using the ASLK board, you will have to use additional R and C (not available on board) on the small breadboard provided




Step 3

Experiment Setup

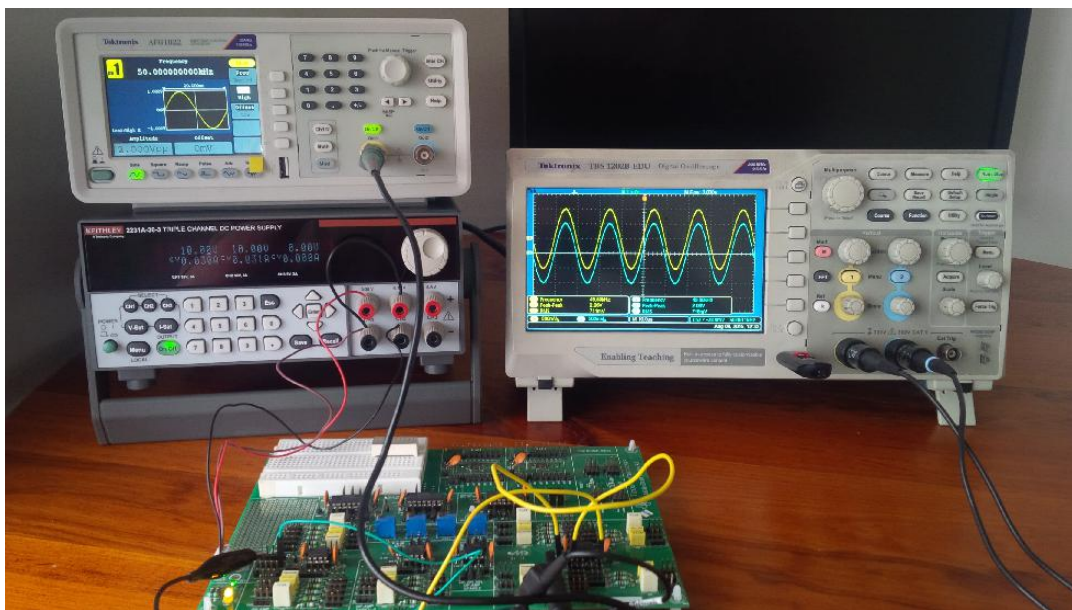- Make the arrangement as shown in figure below -



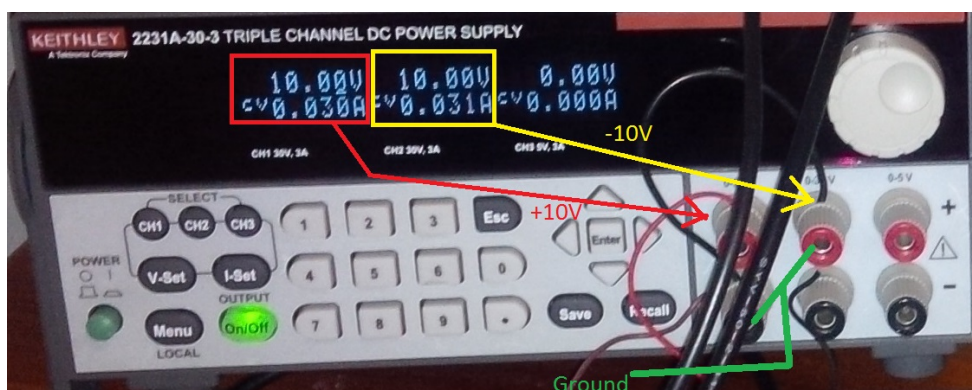- Turn on the DC power supply, ensure that +/- 10V is applied to ASLK /Opamp circuit
 - You can use '2 channels' of 2231A DC power supply in independent mode and combine negative one channel with positive of other to be treated as common or ground point



- Use signal from AFG/signal generator to feed to opamp input
- Probe at input and output pins of the filter to view the signal on oscilloscope - View input on channel 1 and output on channel 2

Step 4


Make the Circuit Work

- Use signal from AFG/signal generator to feed to opamp input
- Set sinusoidal signal from channel 1 of the AFG
 - amplitude = 1 V_{pp}
 - frequency = 50 Hz
- Autoset the oscilloscope to see both input and output waveforms


Step 5

Taking the Measurements

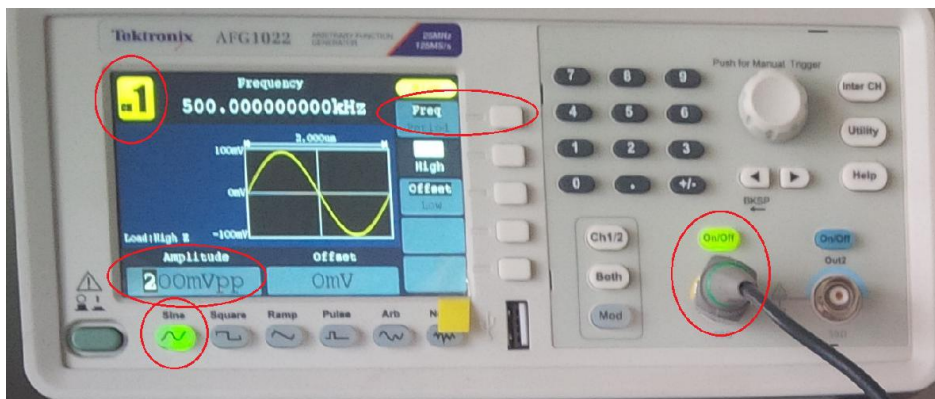- Set input
 - Sinusoidal, 1V peak-to-peak amplitude
 - 1 Hz frequency
 - Continuous mode (on AFG)
 - enable the channel 1 output on AFG



- Autoset the oscilloscope to optimally see both input and output signal
- Set up following measurements:
 - On Ch1 - V_{pp}, V_{rms}, Frequency
 - On Ch2 - V_{pp}, V_{rms}, and Phase (between Ch1 and Ch2)
- Keeping the amplitude of the sinusoid input fixed at 1V peak-to-peak, vary its frequency from 1Hz to 50kHz. You may take more readings near cut-off frequency.
- Tabulate the measurements. You can also capture screenshot for each measurement set.

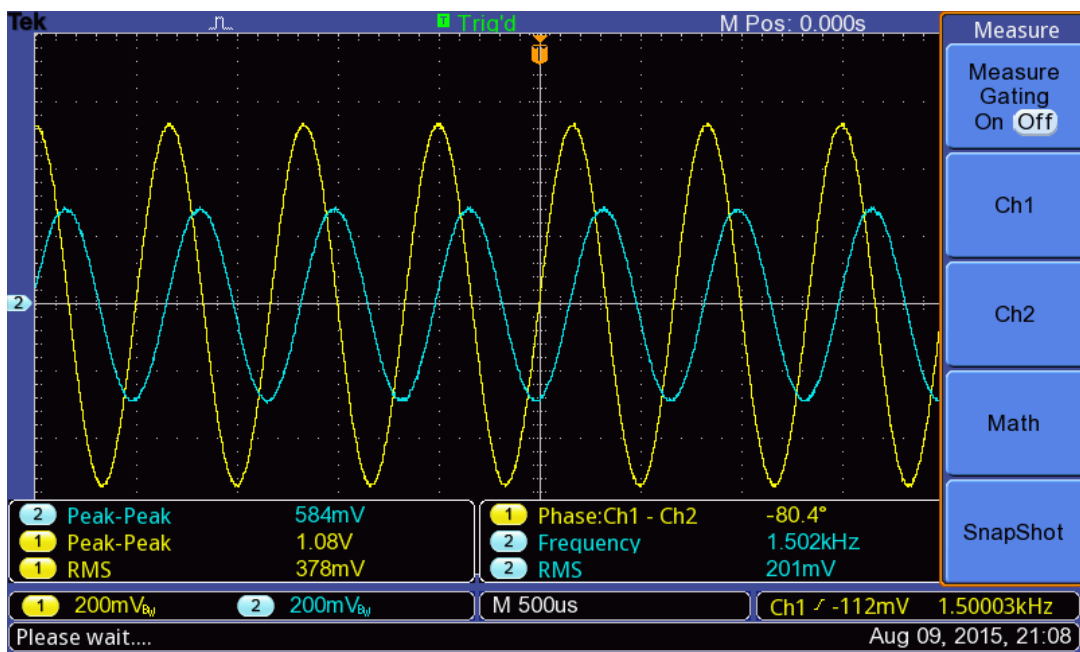

Step 6


Analyzing the Result

- The observation table would look like as shown below. Calculate voltage gain (observed from measurements) and its decible equivalent.

| # | Frequency (Hz) | INPUT | | OUTPUT | | Phase Difference (Degrees) | Voltage Gain | Voltage Gain (dB) |
|----|----------------|---------|-----------|---------|-----------|----------------------------|--------------|-------------------|
| | | Vpp (V) | Vrms (mV) | Vpp (V) | Vrms (mV) | | | |
| 1 | 1 | 1.030 | 358 | 1.03 | 357.0 | 0.00 | 1.00 | 0.00 |
| 2 | 5 | 1.030 | 358 | 1.02 | 356.0 | 0.00 | 0.99 | -0.08 |
| 3 | 10 | 1.030 | 358 | 1.02 | 356.0 | -0.07 | 0.99 | -0.08 |
| 4 | 20 | 1.030 | 358 | 1.02 | 356.0 | -0.08 | 0.99 | -0.08 |
| 5 | 50 | 1.030 | 358 | 1.020 | 356.0 | -3.97 | 0.99 | -0.08 |
| 6 | 100 | 1.030 | 358 | 1.010 | 354.0 | -7.20 | 0.98 | -0.17 |
| 7 | 200 | 1.030 | 358 | 1.000 | 350.0 | -14.40 | 0.97 | -0.26 |
| 8 | 500 | 1.030 | 358 | 0.920 | 324.0 | -33.80 | 0.89 | -0.98 |
| 9 | 700 | 1.030 | 358 | 0.872 | 301.0 | -45.90 | 0.85 | -1.45 |
| 10 | 1,000 | 1.050 | 368 | 0.752 | 261.0 | -60.40 | 0.72 | -2.90 |
| 11 | 1,100 | 1.060 | 370 | 0.712 | 248.0 | -64.80 | 0.67 | -3.46 |
| 12 | 1,200 | 1.060 | 372 | 0.680 | 235.0 | -69.90 | 0.64 | -3.86 |
| 13 | 1,500 | 1.080 | 378 | 0.584 | 201.0 | -80.40 | 0.54 | -5.34 |
| 14 | 1,800 | 1.100 | 384 | 0.496 | 172.0 | -91.60 | 0.45 | -6.92 |
| 15 | 2,000 | 1.100 | 388 | 0.456 | 156.0 | -95.70 | 0.41 | -7.65 |
| 16 | 2,500 | 1.130 | 396 | 0.360 | 121.0 | -108.00 | 0.32 | -9.94 |
| 17 | 3,000 | 1.150 | 402 | 0.280 | 96.7 | -116.00 | 0.24 | -12.27 |
| 18 | 5,000 | 1.190 | 413 | 0.138 | 44.0 | -138.00 | 0.12 | -18.71 |
| 19 | 10,000 | 1.210 | 420 | 0.052 | 13.1 | -162.70 | 0.04 | -27.34 |
| 20 | 20,000 | 1.220 | 422 | 0.022 | 4.4 | -175.00 | 0.02 | -34.88 |

** MINUS sign in the phase signifies that output lags input

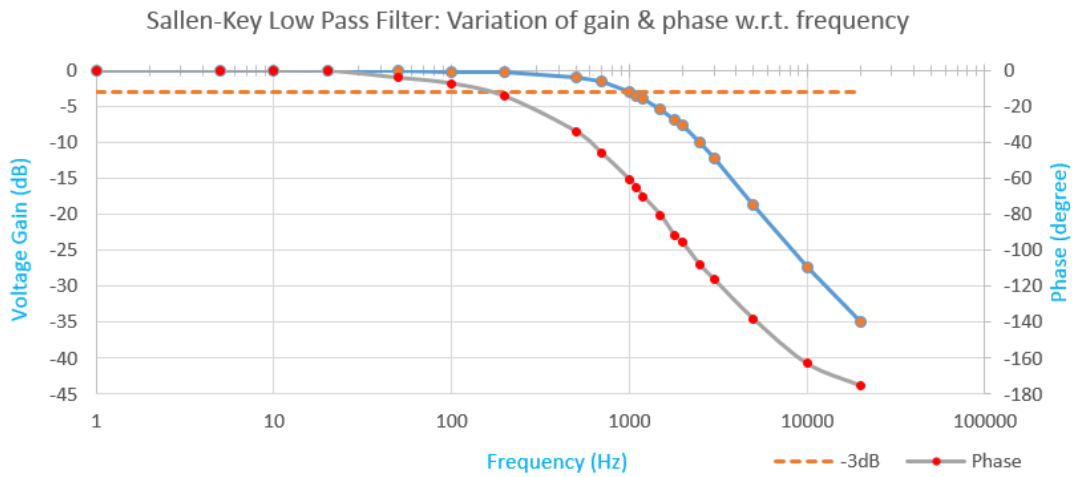- Prepare Bode plot - plot voltage gain and phase against frequency.



- Find out the cut-off frequency from the plot (where the gain drops to -3dB from its passband value)

Step 7

Conclusion

The analysis of the observed results confirm that (As expected):

- The voltage gain of the filter circuit reduces as input frequency is increased
- The roll-off is -40dB/decade as it is a 2nd order filter
- The cut-off frequency (where gain is -3dB or 3dB down from its passband value) is 1000Hz.
- At the estimated (calculated from R and C values) cut-off frequency of 1592 Hz, the gain is down by ~ 6dB and phase is - 90 degrees. (minus sign in the phase signifies, output lags input)