

# Sound\_Sensor\_Module -- Overview



**Mukesh Soni**  
Researcher / PhD Student  
Mechanical Engineering Department  
The University of Melbourne



## Understanding Sound Sensor Module

### Objectives:


After performing this lab exercise, learner will be able to:

- Understand the working of sound sensor module (FC-04)
- Practice working with measuring equipment and laboratory tools like digital oscilloscope and DC Power Supply
- Use digital oscilloscope to debug/analyze the circuit
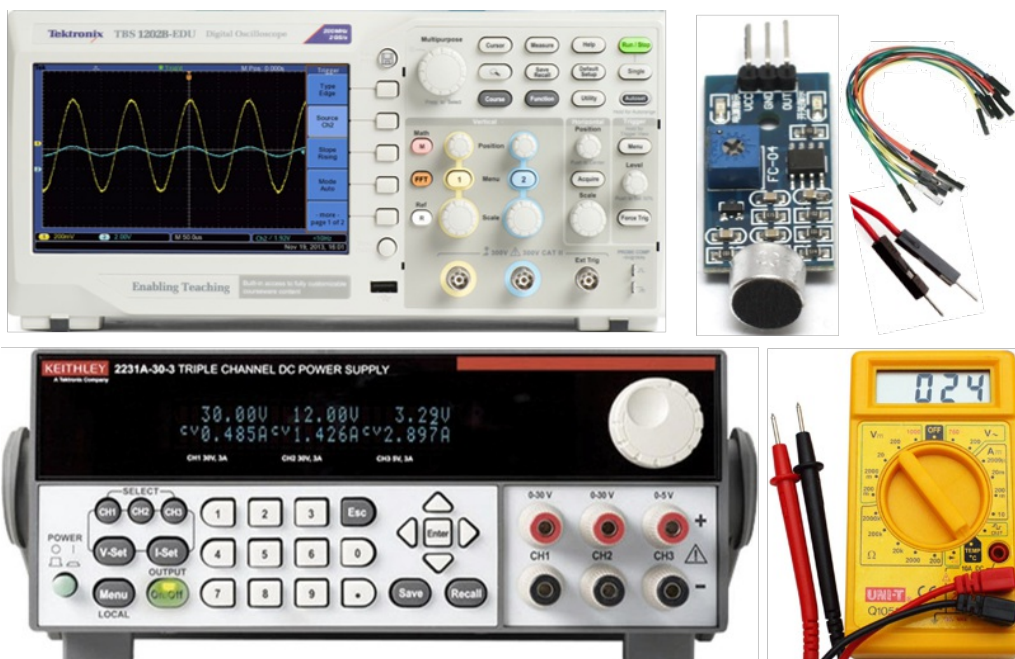
### Equipment:

To perform this lab experiment, learner will need:


- Digital Storage Oscilloscope (TBS1000B-Edu from Tektronix or any equivalent)
- Power Supply (2231A-30-3 Power Supply from Keithley or any equivalent power supply capable of supplying +/- 10V DC)
- Multimeter (for voltage measurement)
- Sound Sensor module FC-04
- Breadboard and connecting wires


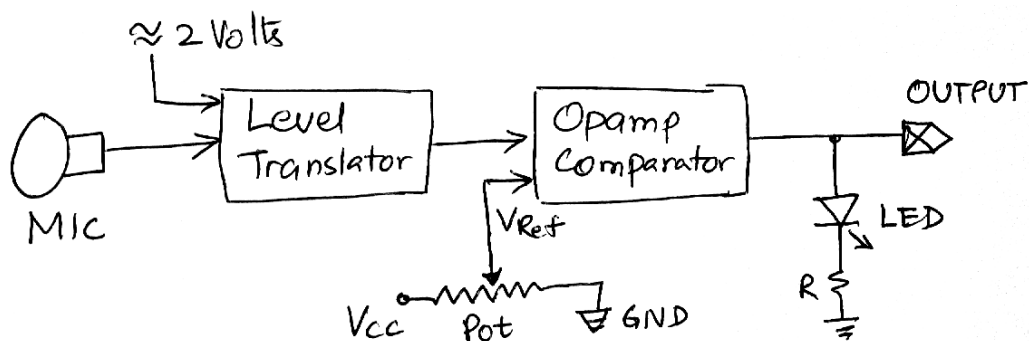
### Theory / Key Concepts:

Before performing this lab experiment, it is important to learn following concepts:

- Sound sensor module FC-04 uses a microphone that converts the acoustic signal (sound) to electrical signal.
- The functional block diagram for FC-04 module is shown below:



- Electrical signal from microphone (which is proportional to sound) is translated at about 2V using potential divider circuit.
- Signal is then amplified and compared (using LM393 Opamp) against a reference to produce a digital output whenever sound signal is more than reference (threshold).
- The threshold can be adjusted using a potentiometer.

## Sound\_Sensor\_Module -- Procedures

### Step 1

#### Check Your Understanding:

Before performing this lab experiment, learners can check their understanding of key concepts by answering these?


- Microphone is used to convert:
  - Sound to electrical signal
  - Light to electrical signal
  - Pressure to electrical signal
  - Distance to electrical signal
- A microphone, connected at non-inverting terminal of an opamp comparator, produces 2.7V. If the reference voltage at inverting pin is 2.2V, then what will be the comparator output ?
  - Voltage close to  $V_{CC}$
  - Voltage close to ground
  - 2.2V
  - 2.7V
- What is the purpose of providing potentiometer on FC-04 sound sensor module?
  - To adjust brightness of output LED
  - To adjust DC power to LM393 comparator
  - To adjust threshold & sensitivity of the switching by sound

- To adjust the level translation of microphone output

## Step 2
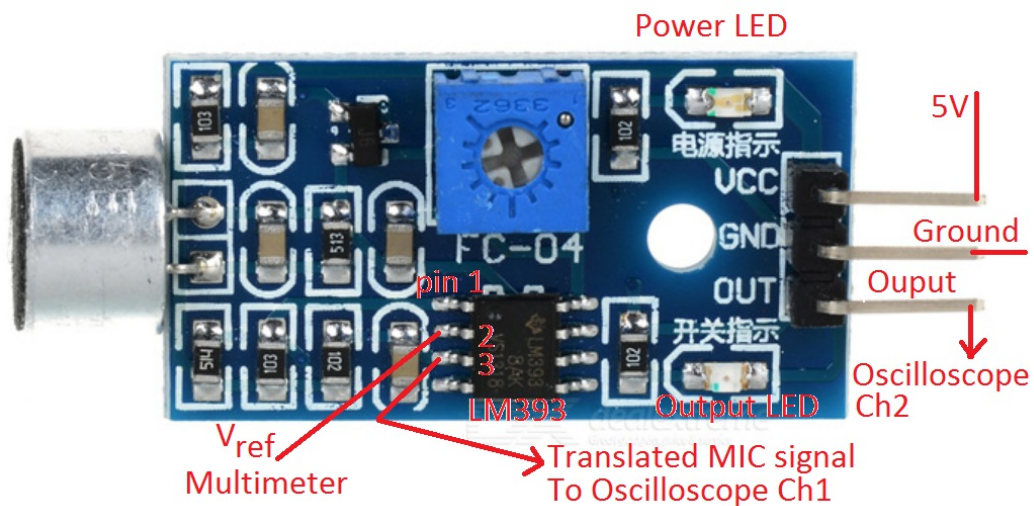
### Circuit diagram / Connection Details


- Using the jumper / connecting wires prepare the circuit as shown below -
  - Pin 3 (MIC output after level translation) of LM393 goes to Ch1 of the oscilloscope
  - Pin 2 ( $V_{ref}$ ) is measured by mutimeter
  - Output pin goes to Ch2 of the oscilloscope
  - 5V is applied between  $V_{CC}$  and Ground using DC power supply



## Step 3
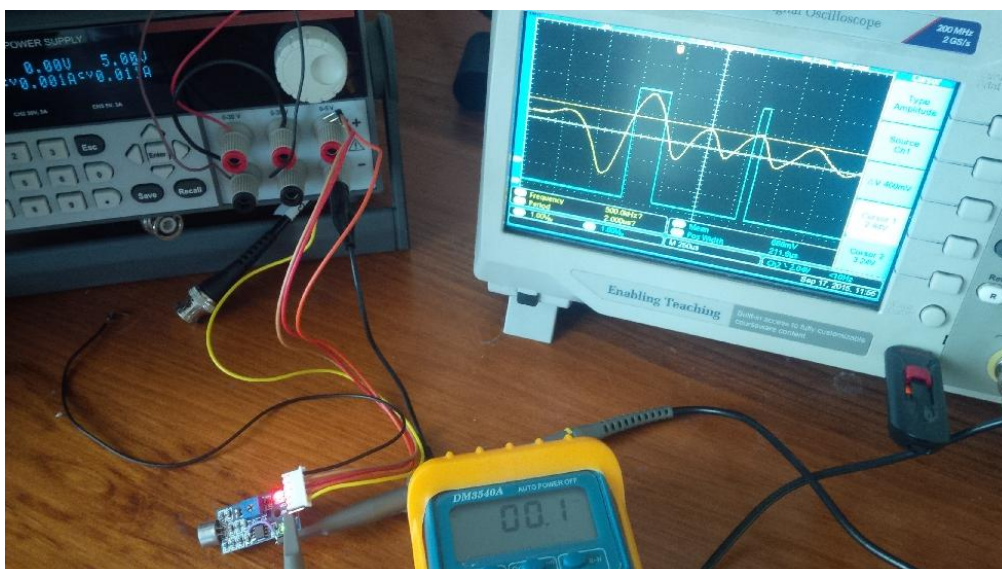
### Experiment Setup

- Make the arrangement as shown in figure below -




- 5V supply is provided using 2231A power supply to the sound sensor module
- From the sound sensor module, Pin 3 of LM393 IC is fed to channel 1 of the oscilloscope
- Connect output pin of sensor module to channel 2
- Multimeter is used to measure the  $V_{ref}$  (voltage at pin 2 of the LM393 IC on sensor module)

## Step 4
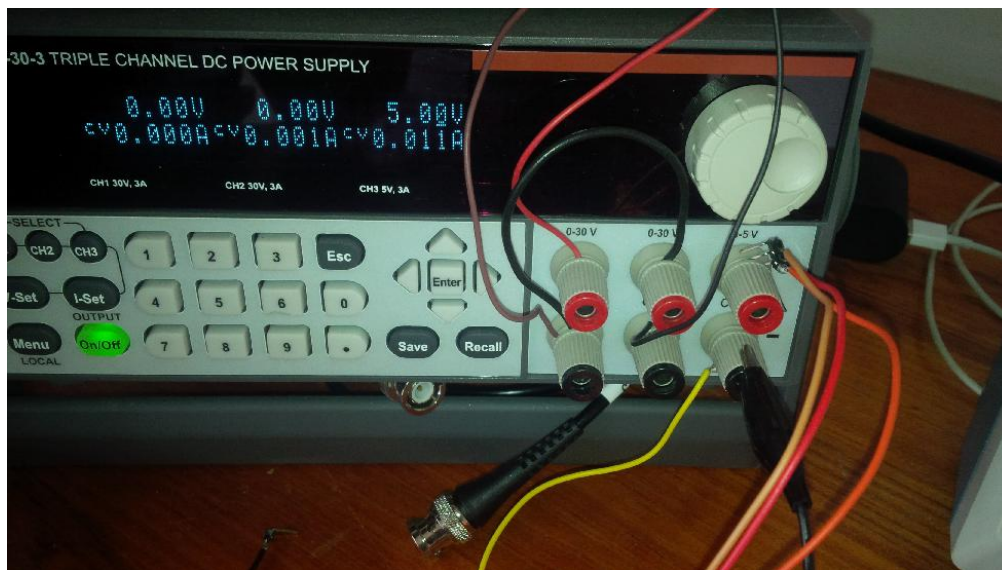
### Make the Circuit Work

- Make sure 5V DC is supplied to the sensor module and its power LED is on - Use Channel 3 of 2231A power supply



- Turn the 'potentiometer' on the sensor module such that the output LED on the module glows without any sound.
- Then turn it in opposite direction so that LED is off for no sound input
- Make a sound by clapping or speaking -- output LED should glow

## Step 5

### Taking the Measurements


- Tune the potentiometer so that output LED is always off.
  - Measure the voltage at pin 2 of the LM393 IC on sensor module using multimeter - This will be the ref voltage



- Set up following measurements:
  - Mean voltage on Ch1 and Ch2
  - Cursor on Ch1 (MIC output)
- Without making any sound, acquire signal and measure mean value of Ch1 and Ch2.
- When Ch1 amplitude (MIC signal) is less than  $V_{ref}$ , the output (Ch2) will be low (0V).



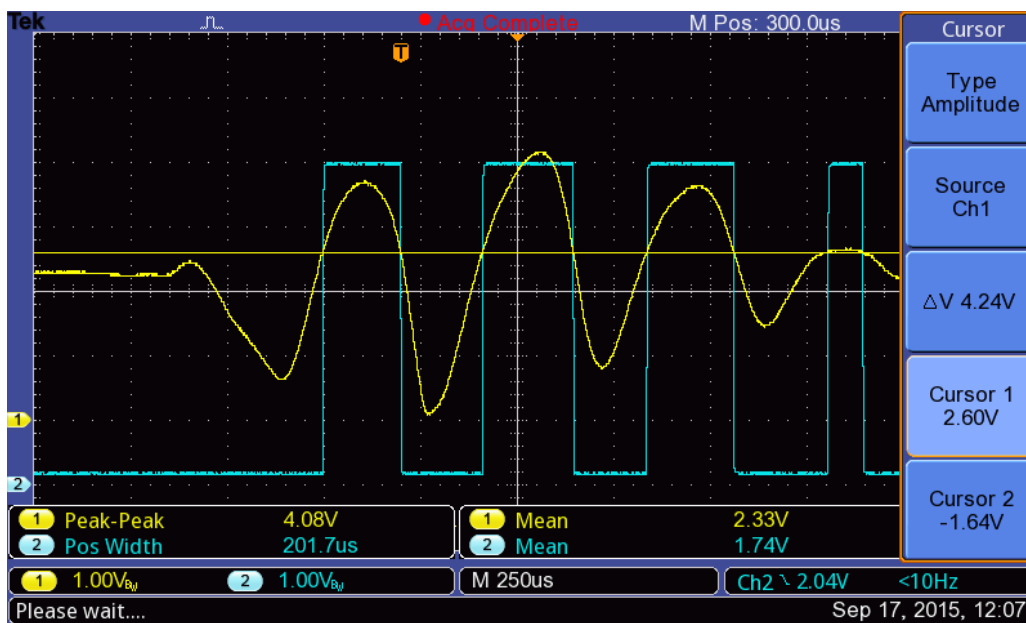- Tabulate the measurements.
- Now make a sound - clap! Capture the transition of output from low to high. User cursor to measure the voltage of Ch1 at which transition happens.



- Repeat the exercise by changing the  $V_{ref}$  to a lower value (say 1.7V) and verify the output transition.

## Step 6

### Analyzing the Result

- The observation can be summarized as below:

Sound input	Ch1 (MIC -Pin 3 of LM393) Voltage	$V_{ref}$ (Pin 2 of LM393) voltage	Ch2 (Output of sensor module) Voltage	Output Transition Level (oscilloscope cursor)	Remarks
No	Mean = 2.27, Pk-Pk = 120mV	2.594	0.000	Not Applicable	Output is normally low without sound input
Yes	Mean = 2.33, Pk-Pk = 4.08V		5.000	2.600	When sound makes transition beyond $V_{ref}$ , output is high
No	Mean = 2.27, Pk-Pk = 80mV	1.760	5.000	Not Applicable	Output is normally high without sound input
Yes	Mean = 2.23, Pk-Pk = 3.04V		0.000	1.750	When sound makes transition below $V_{ref}$ , output is low

## Step 7

### Conclusion

The analysis of the observed results confirm that (As expected):

- Microphone on the sound sensor module picks up sound and compares it against a set threshold or  $V_{ref}$
- If the  $V_{ref}$  is lower than MIC signal, the output is high and vice versa.
- Using potentiometer, we can change  $V_{ref}$  and hence the sensitivity or the output switching