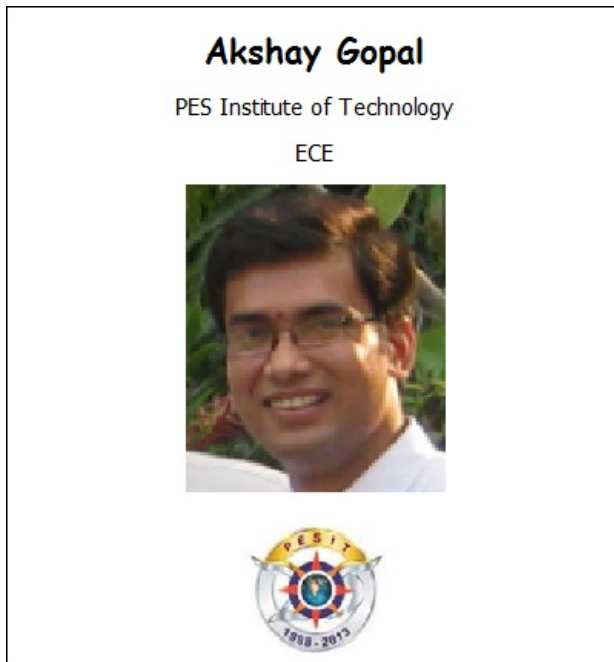


Voltage Divider Bias -- Overview



Lab Overview

After performing this lab exercise, learner will be able to:

- Design Voltage Divider biasing circuit
- Verify the DC conditions
- Build the circuit and observe the output

Equipment

To carry out this experiment, you will need:

- TBS 1000B-EDU Oscilloscope from Tektronix.
- Voltage probe (provided with oscilloscope) / BNC cables
- Breadboard and connecting wires
- Circuit components - Resistor, Transistor SL 100, Regulated DC supply 0-30V DC, Multimeter (for testing)

Theory

- Value of β or h_{FE} of transistors change with temperature and also changes from transistors to transistors. (For SL 100, β varies from 50 to 300).
- This changes the Q point and will result in poor stability. In voltage divider circuit, dependence of Q point on β is reduced and with proper design Q point can be made independent of β .
- Two methods are used to analyze this circuit. viz exact method which can be applied to any voltage divider bias circuit and second one is approximate method where calculation are simplified if βR_E

>10R2.

Design

Q point equations:
Exact Analysis

$$I_B = (V_{th} - V_{BE}) / (R_{th} + (1 + \beta)R_E)$$

where $V_{th} = R_2 * V_{cc} / (R_1 + R_2)$ and $R_{th} = R_1 // R_2 = R_1 * R_2 / (R_1 + R_2)$

$$I_C = \beta I_B$$

$$V_{CE} = V_{cc} - I_C(R_C + R_E)$$

Given $V_{cc} = 10V$, Q point $V_{CEQ} = 5V$ and $I_{CQ} = 2mA$

Measure $\beta = 200$

Assume $V_{BE} = 0.7V$ for silicon diodes

$$V_E = 10\% \text{ of } V_{cc} = 1V$$

Assume $I_E \sim I_C$

$$R_E = V_E / I_E = 1V / 2mA = 500 \text{ Ohm}$$

$$R_C = (V_{cc} - V_{CE} - V_E) / I_C = (10 - 5 - 1) / 2mA = 2k \text{ ohm.}$$

$$V_2 = V_B = V_E + V_{BE} = 1 + 0.7 = 1.7V$$

$$\beta R_E \geq 10R_2$$

$$R_2 = (\beta R_E) / 10$$

$$V_1 = V_{cc} - V_2$$

$$V_1 / V_2 = R_1 / R_2$$

$$R_1 = (V_1 / V_2) * R_2$$

$$R_2 = 1.7V / 90 \mu A = 18.9K$$

$$R_1 = 8.3V / 100 \mu A = 83K$$

Circuit Diagram

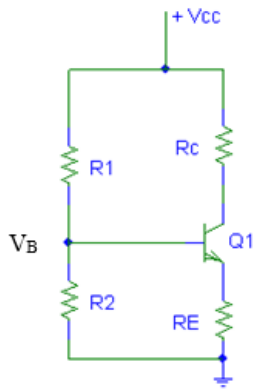


Fig : Voltage divider bias circuit

Voltage Divider Bias -- Procedures

Step 1

Study the circuit, and design the resistors.

Step 2

Place the components on spring board or bread board and connect them as given in circuit diagram figure. Use the springs/patch cords/ wires for connection as required.

Step 3

Set V_{cc} to 10V DC.

Measure DC voltage across

- Collector and emitter of transistor (V_{CE})
- Across the resistor R_c (V_{RC})
- Across the resistor R_2 (V_B or V_{R2})
- Across the resistor R_E (V_E)

Step 4

Calculate the value of I_B , I_E and I_c using equations

$$I_2 = V_B / R_2, \text{ and } I_b = 9 * I_B$$

$$I_C = V_{RC} / R_C \quad \text{and} \quad I_E = V_E / R_E$$

Note :- I_C and I_B can be measured directly by connecting mA and μA in series with R_c , and R_B

Step 5

Compare the measured I_B , I_E and V_{CE} and I_C with the design value.

Step 6

Repeat this experiment by changing the transistor.(change in β value).

Step 7

Draw load line and locate Q point for transistor 1

Parameters	Transistor 1 $\beta =$	Transistor 2 $\beta =$	Design Values calculated for transistor 1
I_B			
I_E			
I_{CQ}			
V_{CEQ}			

Step 8

Result

The voltage divider bias circuit with emitter resistor is designed and verified with the given values.