

Your Name  
Operational Amplifiers Lab  
Date Completed

## PRELAB

- Using the data sheet for your operational amplifier, determine the pin number for the following inputs and outputs. Type your answers in Table A.

I/O	Pin Number
V-	
V+	
V <sub>OUT</sub>	
V <sub>CC-</sub>	
V <sub>CC+</sub>	

**Table A. Operational Amplifier Pin Assignment.**

- What are the maximum values for V<sub>CC+</sub> and V<sub>CC-</sub>?
- What are the maximum values for the input voltages?
- What is the nominal input and output resistance of your op amp?
- What is the voltage gain of your amplifier? Express your answer in dB and decimal.
- What is the op amp's CMRR value in dB? What is the value in decimal?
- Using an op amp, design a circuit that would act as a buffer and eliminate the internal 50  $\Omega$  resistance of the function generator. Would this circuit work? (Hint: What would be the output resistance of the circuit?)

## INPUT RESISTANCE

- With the op amp powered down, measure the resistance between V+ and V- and record your measurement in Table B.
- Power up the op amp and measure the resistance between V+ and V-. Record measurement in Table B.
- Record the value of the input resistance in Table B. How do the measurements taken compare to the value from the data sheet? If there is a discrepancy, explain the cause.

	Powered Down	Powered Up	Data Sheet
Input Resistance (k $\Omega$ )			

**Table B. Input Resistance I.**

11. Measure the actual resistance for  $R_1$  and  $R_2$  with the DMM and record their values in Table C.
12. Power up the circuit. Measure the voltage drop across  $R_1$  and  $R_2$ . Record your results in Table C.
13. Calculate and record the currents through  $R_1$  and  $R_2$ .

	Resistance ( $k\Omega$ )	Voltage (mV)	Current (nA)
$R_1$			
$R_2$			

Table C. Input Resistance II.

14. From the data in Table C, calculate  $i_N$ , and record in Table D.
15. Measure and record the value for  $V_-$ .
16. From the data in Table D, calculate and record the input resistance.

$i_N$ (nA)	$V_-$ (V)	Input Resistance ( $M\Omega$ )

Table D. Input Resistance III.

17. How does the input resistance from Table D compare to the values in Table B? If there is a discrepancy, explain the cause.
18. Replace the  $R_1$  and  $R_2$  with  $470 \Omega$  resistors. Repeat Question 11 – 13. Record your results in Table E.

	Resistance ( $k\Omega$ )	Voltage (mV)	Current (nA)
$R_1$			
$R_2$			

Table E. Input Resistance IV.

19. From the data in Table E, would you be able to determine the input resistance of the op amp (would you be able to repeat Questions 14 - 16)? Explain.



